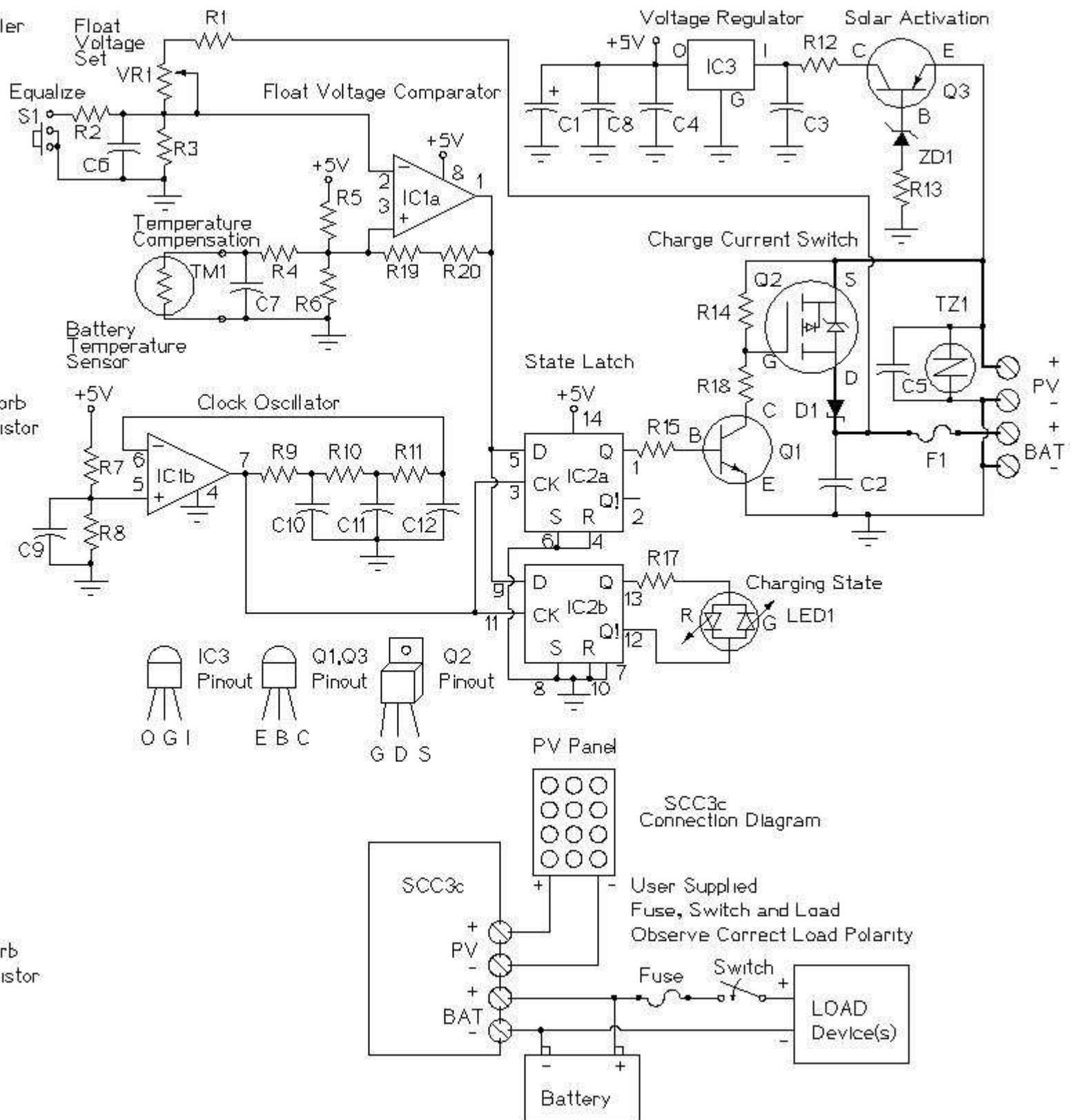


# SCC3 - 12 Volt 20 Amp Solar Charge Controller

A [kit](#) with the circuit board and parts for this circuit is available from [CirKits](#).

CirKits Solar Charge Controller  
Model SCC3c-2 Rev 2  
(c)2008 G. Forrest Cook  
Available in kit form at  
<http://www.cirkits.com/>

- 12V PARTS**  
 IC1 TLC2272CP  
 IC2 CD4013BE CMOS  
 IC3 78L05  
 Q1 2N3904  
 Q2 IRF4905 P-MOS  
 Q3 2N3906  
 D1 20L15T  
 ZD1 1N5242 12V Zener  
 LED1 Red/Green bicolor  
 TZ1 V7270 or V727 Transzorb  
 TM1 2.0K@25c NTC Thermistor  
 F1 20 Amp ATO Fuse  
 VR1 100K 25 turn  
 All resistors are 1/4W  
 R1 270K  
 R2 470K  
 R3 75K  
 R4 180K  
 R5,R7,R8,R9,R10,R11 100K  
 R6 200K  
 R12,R17,R18 330  
 R13,R14 2.2K  
 R15 10K  
 R19,R20 15M  
 C1 470uF 16V  
 C2,C3,C4,C5,C6,C7,C8,C9,  
 C10,C11,C12 100nF
- 24V PARTS (differences)**  
 D1 18TQ045  
 Q1 MPSA05  
 ZD1 1N5252  
 TZ1 V470 or V747 Transzorb  
 TM1 4.6K@25c NTC Thermistor  
 F1 15 Amp ATO Fuse  
 VR1 200K 25 turn  
 R1 620K  
 R12 680  
 R13 4.7K  
 R18 10K



## SCC3 - 12 Volt 20 Amp Solar Charge Controller

(C) 2007, G. Forrest Cook

### Introduction

The SCC3 is a solar charge controller, its function is to regulate the power flowing from a photovoltaic panel into a rechargeable battery. It features easy setup with one potentiometer for the float voltage adjustment, an equalize function for periodic overcharging, and automatic temperature compensation for better battery charging over a wide range of temperatures. The SCC3 is able to handle reverse polarity connection of both the battery and photovoltaic panel.

The design goals of this circuit were efficiency, simplicity, reliability and the use of field replaceable parts. A medium power solar system can be built with the SCC3, a 12V (nominal) solar panel that is rated from 100 milliamps to 20 amps, and a lead acid or other rechargeable battery that is rated from 500 milliamp hours to 400 amp hours of capacity.

It is important to match the solar panel's current rating to the battery's amp-hour rating (C). A typical maximum battery charging current is C/20, so a 100 amp hour battery should have a solar panel rating of no greater than 5 amps. It is advisable to check the battery manufacturer's data sheets to find the maximum charge current. On the other hand, if the solar panel output current is too low, the battery may take too long to charge.

With a few parts changes, it is possible to modify this circuit to work as a 24V/15A solar charge controller. The 24V parts differences are shown on the schematic.

## Specifications (12V version)

Maximum solar charging current: 20 Amps  
Nominal battery voltage: 12V.  
Night time battery current drain: 1.3ma

See the full SCC3 kit [specifications](#) for a more detailed list.

## Theory

The power control circuitry of the SCC3 routes the operating current from the solar panel input through Q3 and IC3. When the solar panel voltage exceeds 12V, zener diode ZD1 conducts and turns on Q3, providing power to IC3. IC3 produces a regulated 5 Volt power source. The 5V is used to power the circuit's logic and as a reference voltage for comparing to the battery float voltage.

The float voltage comparator IC1a compares the battery voltage (divided by R1/VR1 and R3) to a reference voltage (divided by R5 and R6). The comparison point is offset by the thermistor TM1 for temperature compensation. The comparison point is also modified by the Equalize switch, S1 and R2. The output of IC1a goes high (+5V) when the battery voltage is below the float voltage setting. The output goes low when the battery voltage is above the float voltage setting. This provides the charge/idle signal that controls the rest of the circuit.

The charge/idle signal is sent to IC2a and b, a pair of D-type flip-flops. The flip-flops are clocked by the IC1b phase-shift clock oscillator. The clocking causes the flip-flop output to produce a square wave charge/idle signal that is synchronized with the frequency of the clock oscillator. The two halves of IC2 operate in synchronization, IC2a is used to drive the current switching circuitry, IC2b is used to drive the charging state indicator LED either red (charging) or green (floating).

The clocked charge/idle signal switches bipolar transistor Q1 on and off. The Q1 signal is used to switch power MOSFET Q2, which switches the solar current on and off through the battery. The solar charging current flows through the heavy lines on the schematic. Diode D1 prevents the battery from discharging through the solar panel at night. Fuse F1 prevents excessive battery current from flowing in the event of a short circuit. Transzorb TZ1 absorbs transient voltage spikes that may be caused by lightning.

## Alignment

If a battery pack with a float voltage setting below 13V is used with the SCC3 (LiPO or NiMH for example), zener diode ZD1 should be changed to a 1N4740 (10V) and resistor R1 should be changed to 250K.

[ ]CAUTION: Large batteries can produce dangerous currents that can cause burns and fire hazards. Remove loose metal jewelry when working with lead acid batteries. The circuit should be mounted on a panel or in a box using threaded standoffs. Wiring should be securely clamped and there should be no externally exposed bare wiring.

[ ]Connect the board's BAT - terminal to the battery - terminal.  
[ ]Connect the board's BAT + terminal to the battery + terminal.  
[ ]Connect the board's PV - terminal to the solar panel - terminal.  
[ ]Connect the board's PV + terminal to the solar panel + terminal.

[ ]Point the solar panel toward the sun.  
[ ]The bicolor LED should light up as the sun shines on the solar panel. The LED can be red, green, or alternating red and green. The LED must be shaded from direct sunlight to be visible.

[ ]Measure the connected solar panel's voltage with the meter.  
[ ]Measure the battery voltage with the meter.  
The solar panel must be at a higher voltage than the battery for the circuit to charge the battery.  
[ ]Turn the equalize switch off (closest to the board edge).  
[ ]Turn the potentiometer, VR1 25 turns clockwise, The LED should be red.  
[ ]Turn VR1 counter clockwise until the LED starts blinking red and green. The battery voltage is now at the float voltage setting.

[ ]While measuring the battery voltage, adjust VR1 clockwise to align the float voltage set point. If the LED turns red before it reaches the desired float voltage, the battery will need to charge for a while.  
[ ]When the battery is fully charged, it should be at the float voltage and the led should show alternating colors.  
[ ]The float voltage should be set when the board and battery are at room temperature. Typical 12V set points are 13.8V for a gell cell and 14.5V for a wet cell.  
Follow your battery manufacturer's recommendations for the optimal float voltage setting.  
[ ]Adjust the float voltage again, after the battery has become fully charged and the LED is green with occasional red flashes.

## Use


Connect the solar panel to the SCC3 PV terminals, connect the battery to the SCC3 battery terminals.

Put the solar panel in the sun, the battery will charge up. In systems where the battery is frequently deep-discharged, the equalize switch should be occasionally turned on for a period of several hours to a full day.

When the battery is low and the sun is shining, the LED will be red. As the battery reaches the float voltage, the LED will alternate red/green. When the sun goes down, the LED will shut off.

## SCC3 Circuit Extensions

## Secondary Battery Charger

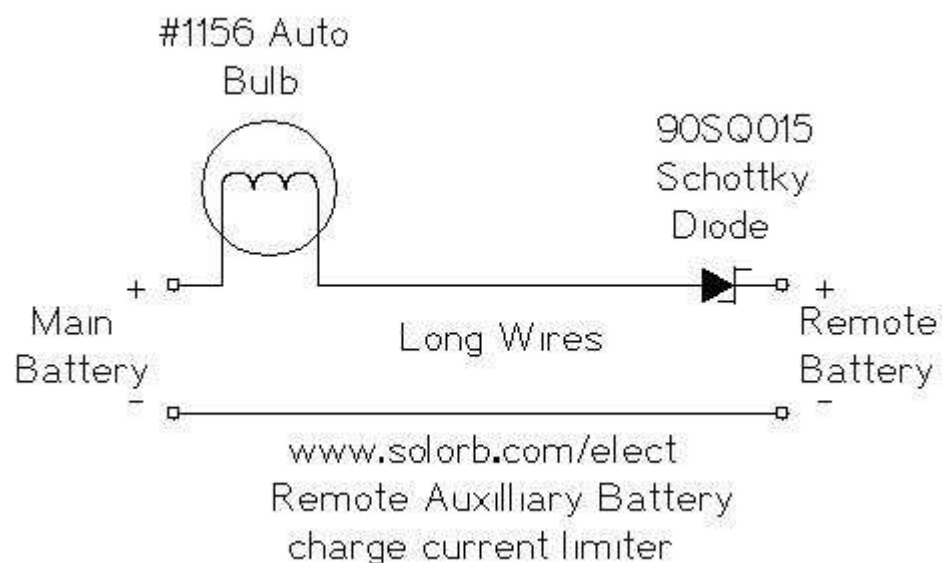

The above circuit may be used if you wish to charge a remote secondary battery. The #1156 lamp limits the secondary battery's charge current to a maximum of 2 amps, it also protects the remote wiring from high currents in the event of a short circuit. The wiring should be rated to handle more than 2 amps of current, #16 or #14 gauge wire is recommended. Other lamps may be used for setting different maximum charge current values. The Schottky diode prevents a load on the main battery from discharging the secondary battery. The diode has a .5V drop, so the secondary battery will always stay .5V below the main battery's maximum (float) voltage setting. A wet cell lead acid main battery and a gell cell secondary battery will work well in this configuration. Float voltages for gell cell batteries are lower than for wet cell batteries.

## Dump Load Controller

A [Dump Load Controller](#) circuit can be used to feed excess solar power to an auxilliary load such as a heating resistor. The dump load circuit can be constructed from a second SCC3 kit using custom wired jumpers. The dump load circuit monitors the PV voltage. When the PV has charged the battery and the battery reaches the SCC3 float voltage setting, the SCC3 PV circuit opens up and the PV voltage rises. The dump load circuit detects this higher PV voltage and connects the dump load to the PV.

For 12V systems, the dump load circuit should be adjusted so that it activates at a PV voltage of around 15V. The dump load resistor should be connected across the terminals labeled "Dump" in the schematic. For the optimal dump load power transfer, the value of the dump load resistor should be chosen so that it pulls the PV voltage down to the PV panel's rated maximum power point during full sun conditions. The dump load resistor should have a power rating that is greater than the PV panel's maximum output wattage rating. If a dump load other than a resistor is used, the load should be able to run with short pulses of DC energy. Dump load power is only available when the main battery becomes fully charged.

## Solar Charge Controller Kits For Sale

A kit version of this solar power center circuit is available from [CirKits](#).

buying the kit saves you a lot of trouble locating parts and wiring the circuit.

