

2Channel + Microphone Stereo Mixer

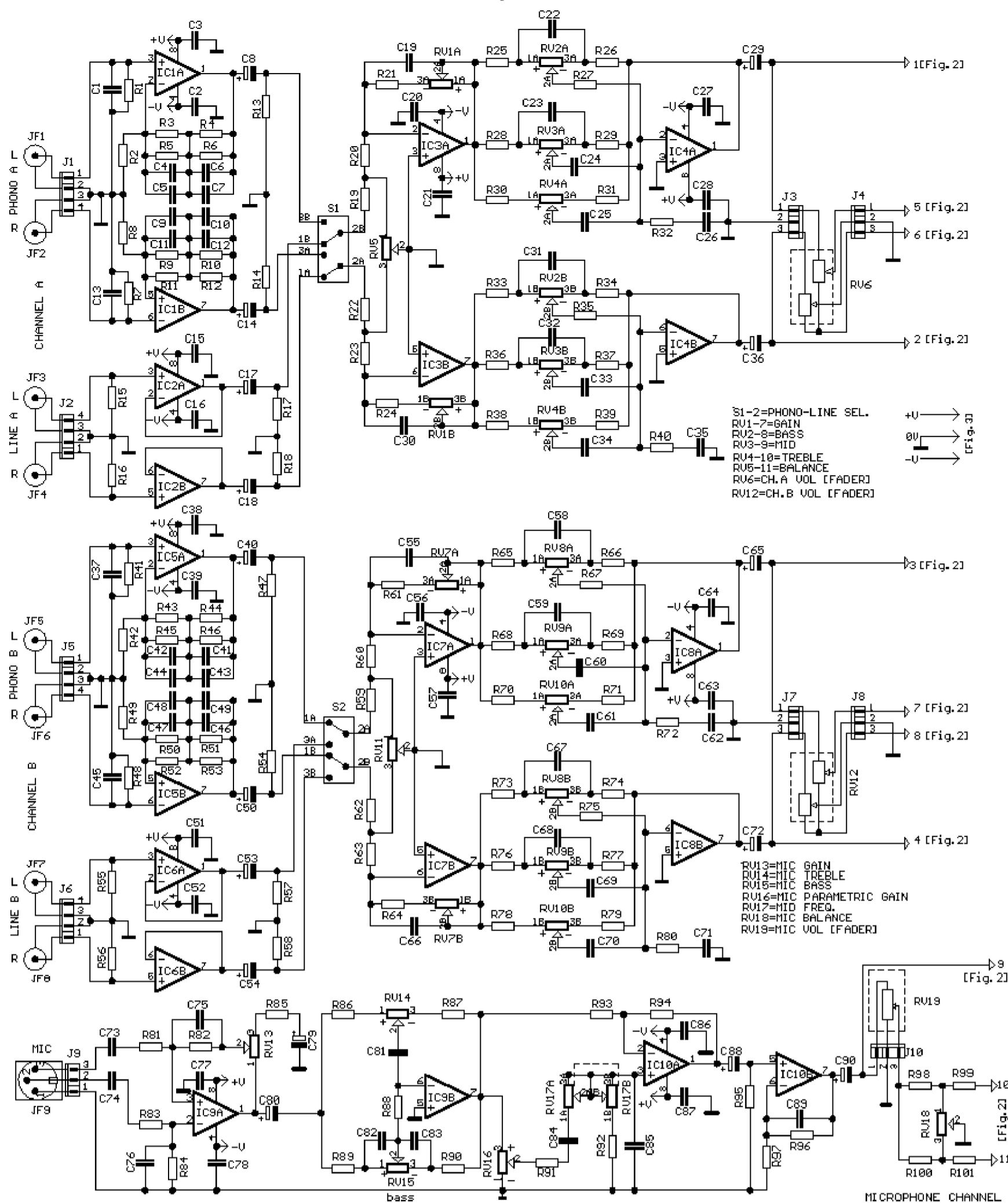


Fig.1--2 STEREO+LMIC CHANNEL MIXER PROJECT [PART 1]

Sam 9/82

A lot of friends me asked to draw a more shrunk circuit 2-ch mixer, which will contain also, operation CROSSFADER. The circuits can be modified and added also other channels, repeating basic that I give. It can be added channels stereo PHONO/line or even channels microphone with proportional modification of next stages. In the Fig.1 exist the input circuits of two channels and input of microphone channel. The two basic channels she is same between them. Thus that it□□ go for a channel, the he is also go for the other. In each stereo channel exist two inputs, classic stereo input PHONO that is practical a correction filter RIAA and concerns the signal amplification of sound that emanates from the classic reproduction heads of classic disks LP. Exist also a stereo input of LINE □□high level□□ for signals that emanate from CD players, Tuners, DVD, etc. The exits of this two stages are selected with switch S1 or S2 and they are applied in the next stage which is constituted from adder IC3. Here is regulated the BALANCE with the RV5 and GAIN with the RV1. In the next stage round the IC4 exist a classic 3-band regulation of tone circuit, the regulation of which becomes with the RV2-3-4. The exit of IC4 drive the RV6 that is at preference pontesometer [FADER]. By points 1-2-5-6 the signals connected to next stage [Fig.2]. In the Fig.1 exist also the microphone input, which is in electronic Balance connection, round the IC9A. Here exist the regulation of GAIN with the RV13. It follows a stage of tone two-band regulation, round the IC9B and a stage of parametric regulation of mid band with RV16 [Gain] and RV17 [Frequency Band]. With the RV19 we regulate VOLUME [FADER] and with the RV18 we regulate the BALANCE. By points 9-10-11 the signal is connected to the corresponding points that are found in the Fig. 2.


Part List [Fig.1]

R1-7-15-16-41-48-55-56=47 Kohms
 R2-8-42-49=150 ohms
 R3-5-9-11-43-45-50-52=180 Kohms
 R4-6-10-12-44-46-51-53=15 Kohms
 R13-14-17-18-47-54-57-58-95=100 Kohms
 R19-22-59-62-98-100=4.7 Kohms
 R20-23-60-63-21-24-61-64=10 Kohms
 R25-26-33-34-65-66-70-71=10 Kohms
 R27-35-67-73-74-75-78-79-96=10 Kohms
 R28-29-36-37-68-69-76-77=3.3 Kohms
 R30-31-38-39-70-71-78-79=1.8 Kohms
 R32-40-72-80=330 ohms
 R81-83=2.2 Kohms
 R82-97=6.8 Kohms
 R84-88-93-94=22 Kohms
 R85=100 ohms
 R86-87=2.7 Kohms
 R89-90=5.6 Kohms
 R91-92=3.9 Kohms
 R99-101=10 Kohms

C1-13-37-45=150pF mylar-ceramic
 C2-3-15-16-20-21-27-28-38-39=47nF
 C4-5-9-11-42-44-47-48=18nF
 C6-10-41-46=3.9nF
 C7-12-43-49-82-83=5.6nF
 C8-14-17-18-40-50-53-54-88=10uF 16V
 C19-30-55-66-89=22pF
 C22-31-58-67=47nF
 C23-32-59-68-25-34-61-70-85=4.7nF
 C24-33-60-69=22nF
 C26-35-62-71=1.2nF
 C29-36-65-72-80-90=10uF 16V
 C56-57-63-64=47nF
 C73-74=1uF 100V MKT
 C75-76=68pF ceramic or mylar
 C77-78-86-87=47nF
 C79=47uF 16V
 C81=2.2nF
 C84=10nF
 S1-2=2X2 0N/ON SW

IC1-5-9-10=**NE5532-LM833**
 IC2-3-4-67-8=**TL072**
 RV1-7= 22 Kohms Log. pot.*
 RV2-3-8-9=2X100 Kohms Lin. pot.*
 RV4-10=2X470 Kohms Lin. pot.*
 RV5-11-18=10 Kohms Lin. pot.*
 RV6-12=2X22 Kohms Log. pot. 45mm Slider [FADER]
 RV13=10 Kohms Log. pot.*
 RV14-15-16=47 Kohms Lin. pot.*
 RV17=2X100 Kohms Log.pot.*
 RV19=10 Kohms Log. pot. 45mm Slider [FADER]
 J1-2-5-6=4pin conn. 2.54mm pin step
 J3-4-7-8-9-10=3pin conn. 2.54mm pin step
 Jf1...8=RCA female Jack
 JF9=3pin XLR male

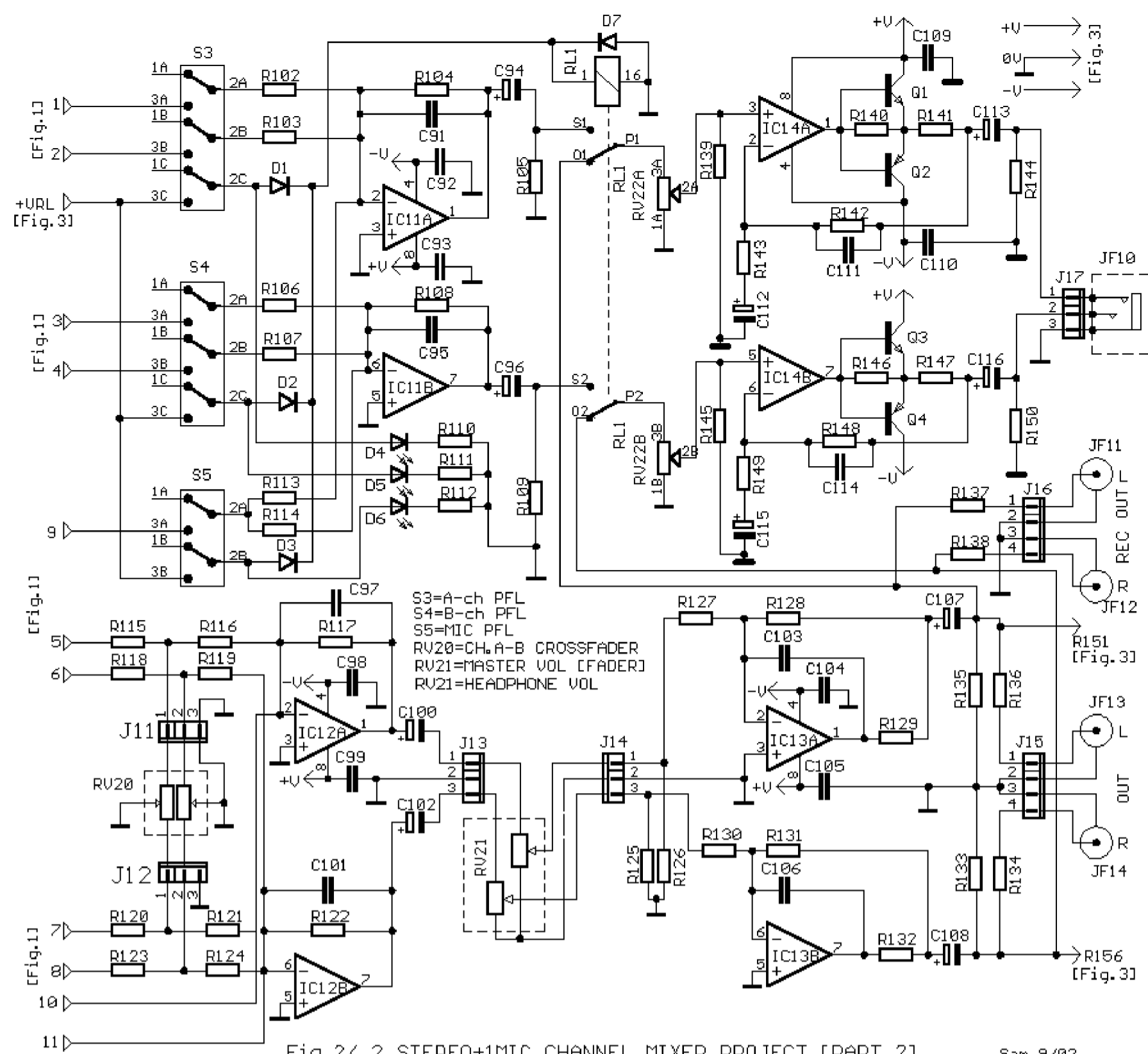*ALPS or PIHER type Potentiometer
 All the Resistors is 1/4W 1% metal film
 All the [nF] capacitors is 63-100v 5% MKT



In the Fig.2 about the various signals that emanate from the Fig.1. Switches S3-4-5 execute the operation of pre-Fader-listen [PFL] of proportional channels. If some switch functions then turns on corresponding diode led D4-5-6. Simultaneous turn-on the relay RL1 disconnect the program in the headphone and supply with the PFL signal. Round the IC14 exist the amplifier circuits of headphone drive. Round the IC12 exist the addition circuit of the signals from the two channels and the mic channel, as well the RV20 which function as CROSSFADER between the two stereo channels. The RV21 is final MASTER VOLUME [FADER] and adjust the final percentage of signal to the output. This role undertake the IC13 that has the leading possibility via the outputs Jf13-14 a power amplifier, simultaneously from the exits Jf11-12 we can take signal for recording.

Part List [Fig.2]

R102-103-106-107-113-114=10 Kohms
 R104-108-117-122-125-126=22 Kohms
 R105-109=1 Mohms
 R110-111-112=1 Kohms
 R115-118-120-123-127=10 Kohms
 R116-119-121-124-130=10 Kohms
 R128-131=27 Kohms
 R129-132-137-138-140-146=100 ohms
 R133-135-139-145=100 Kohms
 R134-136=47 ohms
 R141-147=10 ohms
 R142-148=4.7 Kohms
 R143-149=820 ohms
 R144-150=47 Kohms

RV20=2X22 Kohms Log. pot. 45mm Slider [FADER]
 RV21=2X10 Kohms Log. pot. 45mm Slider [FADER]
 RV22=2X10 Kohms Log. pot.*
 C91-95-97-101-103-106-111-114=22pF
 C92-93-98-99-104-105-109-110=47nF
 C94-96-100-102=10uF 16V
 C107-108-113-116=470uF 25V
 C112-115=47uF 16V
 IC11-12=**TL072**
 IC13-14=**NE5532 - LM833**
 D1-2-3=1N4002
 D4-5-6=LED 3 or 5mm RED
 D7=1N4148
 Q1-3=**BD139**

Q2-4=**BD140**
 S3-4=3X2 PDT ON/ON SW
 S5=2X2 PDT ON/ON SW
 RL1=12V Relay 2X2 SW
 JF10=Jack female stereo 6.3mm
 JF11....14=RCA female Jack
 J11....14-17=3pin conn. 2.54mm pin ste
 J16-17=4pin conn. 2.54mm pin step
 RV20=2X47 Kohms Lin. Slider [FADER]*
 RV21=2X10 Kohms Log. Slider [FADER]*

*ALPS or PIHER type Potentiometer
 All the Resistors is 1/4W 1% metal film
 All the [nF] capacitors is 63-100v 5% MKT

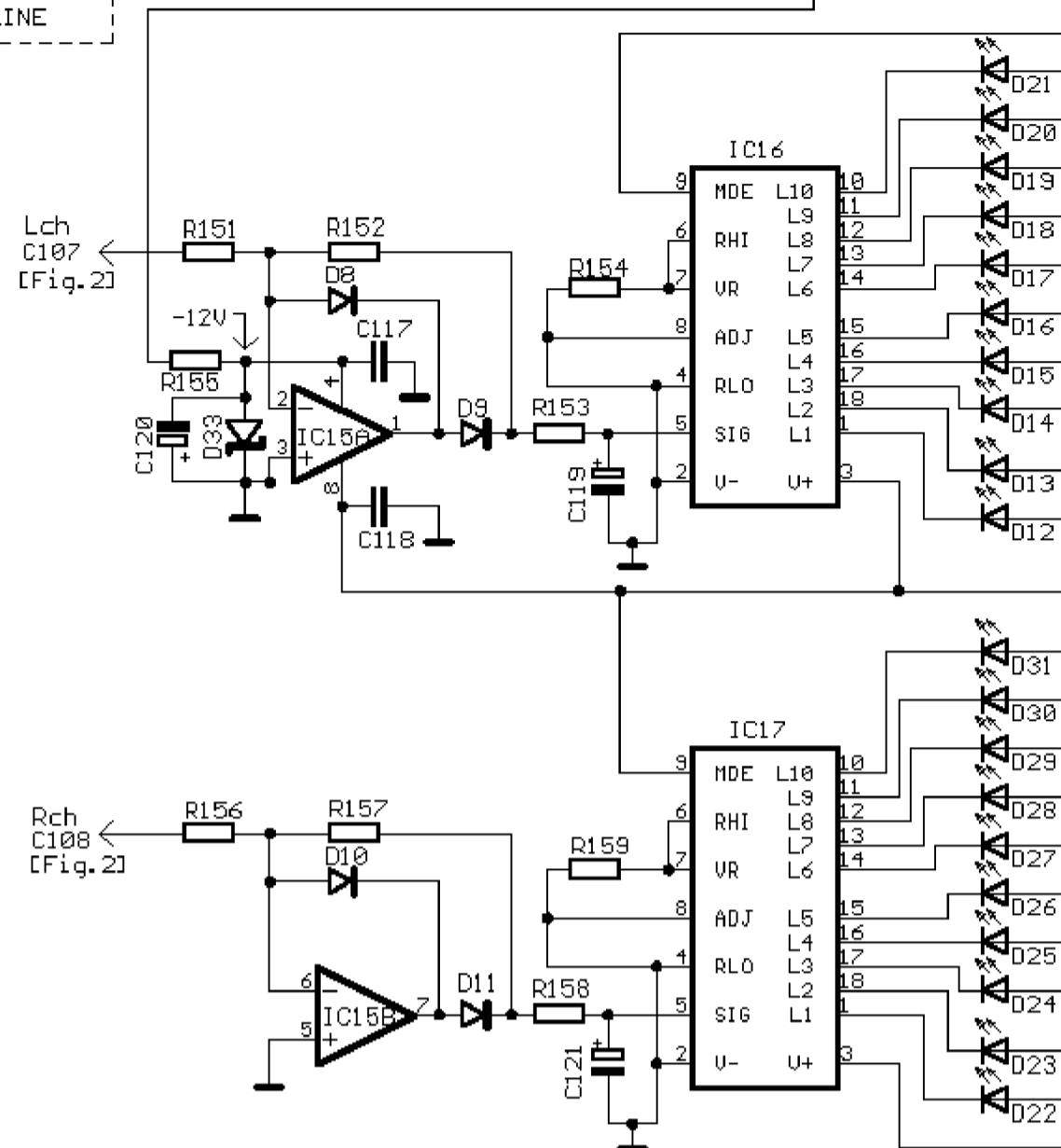
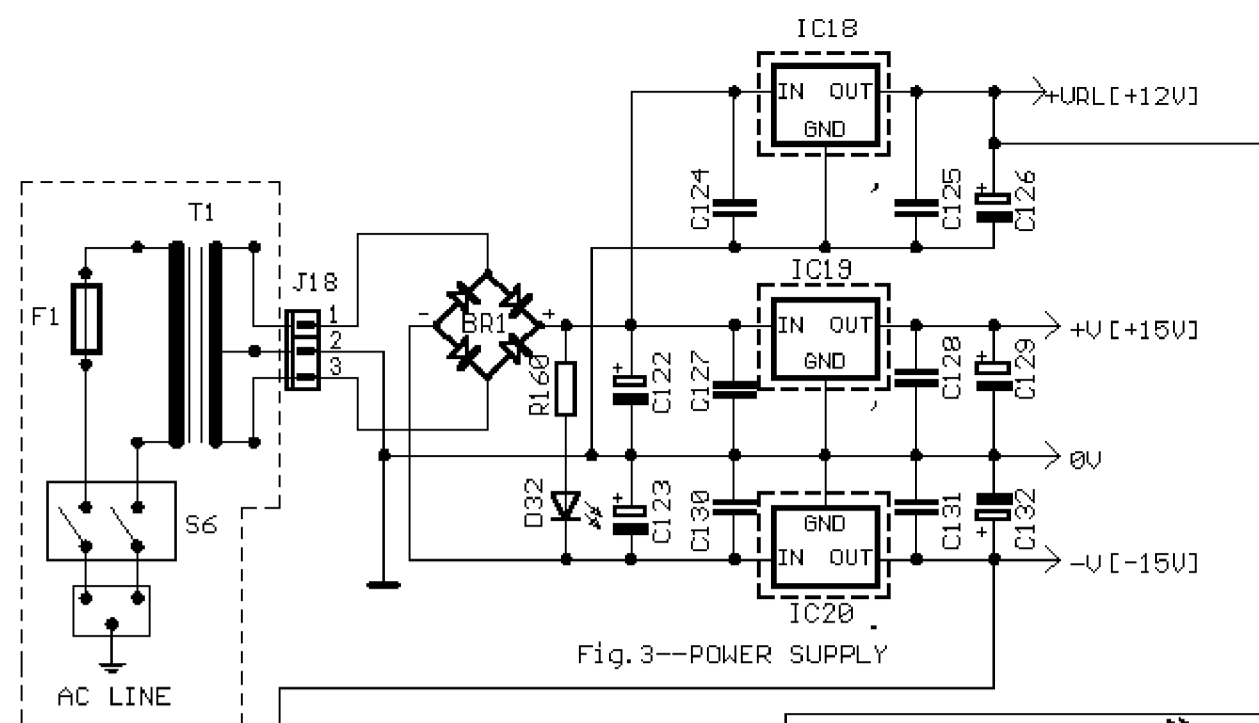


Fig. 4/ 2-ch VUMETER Sam 9/02

In the Fig.3 exist a classic supply circuit and stabilization of various voltages that needs the various circuits of mixer as +/-15V for the Audio department and + 12V for the RL1 and VU meter supplying. The regulators IC18-19-20 good it is they are placed on small heatsinks. Transformer T1 it is placed in a separate box, far from the remainder circuit, so that is not created problem of influence of rests circuits, from noise, unless it is toroidal. In the Fig.4 is found the indication circuit of level. This becomes with two classic circuits round the IC16-17 that drive the diodes Led D12...D31, that portrays the level in steps of 3dB. The IC15 functions as precision rectifier.

Part List [Fig.3-4]

R151-152-156-157=10 Kohms
 R153-154-155-158-159=1 Kohms
 R160=2.7 Kohms
 C117-118-124-125-127-128-130-131=100nF
 C119-121=1uF 25V
 C120=10uF 25V
 C122-123=4700uF 40V
 C126-129-132=19uF 25V

BR1= 80V/3A BRIDGE RECTIFIER
 D8-9-10-11=1N4148
 D12.....31-32=RED LED
 D33=12V 0.5W ZENER
 IC15=TL072
 IC16-17=LM3516
 IC18=7812 on Heatsink
 IC19=7815 on Heatsink

IC20=7915 on Heatsink
 T1=230V//2X15Vac >30VA
 F1=500mA SLOW BLOW FUSE
 S6=2X2 ON-OFF SWITCH
 J18=3pin conn. 3.96mm pin step

All the Resistors is 1/4W 1% metal film
 All the [nF] capacitors is 63-100v 5% MKT

SPECIFICATIONS

PHONO INPUT [Unbalanced RCA]

Sensitivity 2.5mV rms
Impedance 47K//150pF

LINE INPUT [Unbalanced RCA]

Sensitivity 1V rms
Impedance 47K
Gain X1 until X3

3-band EQ 50HZ, 1KHZ, 10KHZ [± 18 dB/oct]

MIC INPUT [Balanced XLR]

Sensitivity -56dB
Impedance 2K
Gain 36dB

EQ. Section

High ± 18 db at 20KHZ
Mid. Freq. 200HZ - 6KHZ
Mid. Gain ± 15 db
Low ± 18 db at 20HZ

HEADPHONE OUT


impedance 100 ohms min.

FREQUENCY RESPONSE 20HZ-20KHZ -2dB

DISTORTION T.H.D 0.01% A 1KHZ

OUTPUT LEVEL +4db Typ.

Block Diagram

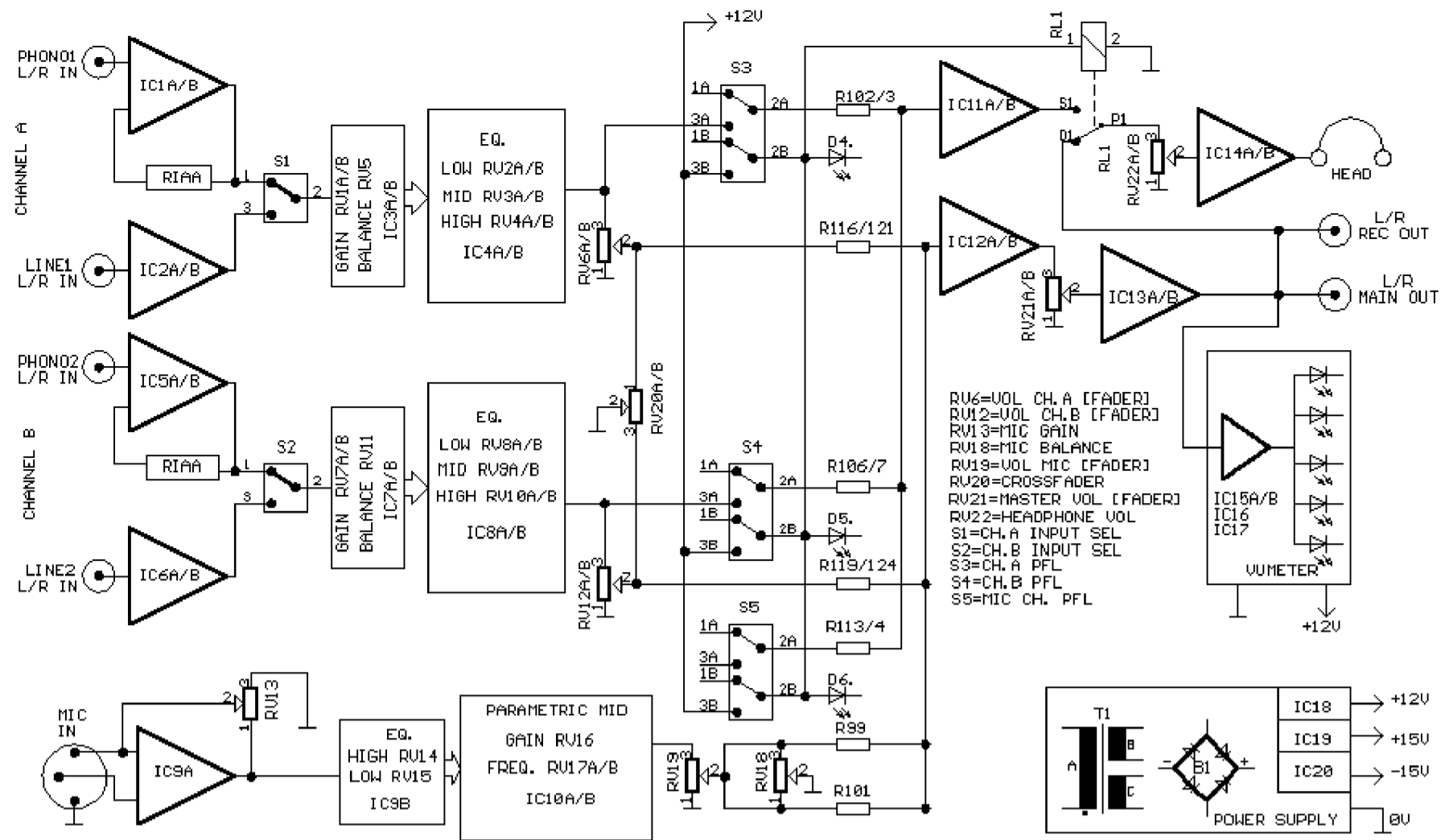

In the Fig.5 appears the block diagram of circuit, which it will help in the comprehension of logic of circuit.

Sam Electronic Circuits 10/02

[Home] [My Database] [My Guestbook]