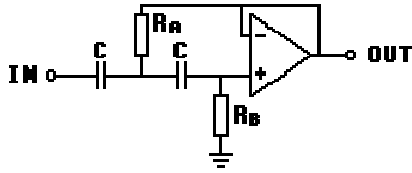


# Active Filter: Bessel (2st order, 12 dB/octave, Highpass)




$$C=4.7\text{n}-10\text{nF}$$

$$R_a=1.1017/(2*\pi*F_c*C)$$

$$R_b=1.4688/(2*\pi*F_c*C)$$

Units:  $R_x$  [Ohm],  $C$  [F],  $F_c$  [Hz]
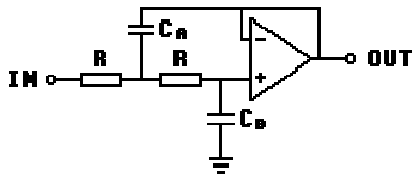
# Active Filter: Bessel (2nd order, 12 dB/octave, Lowpass)




$$R=4.7\text{k}-10\text{kOhm}$$

$$C_a=0.9076/(2*\pi*F_c*R)$$

$$C_b=0.6809/(2*\pi*F_c*R)$$

Units:  $R$  [Ohm],  $C_x$  [F],  $F_c$  [Hz]
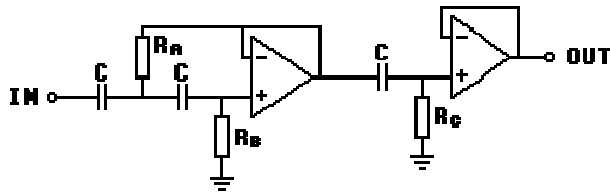
# Active Filter: Bessel (3st order, 18 dB/octave, Highpass)



$$C=4.7\text{n}-10\text{nF}$$


$$R_a=1.0474/(2*\pi*F_c*C)$$

$$R_b=2.0008/(2*\pi*F_c*C)$$

$$R_c=1.3228/(2*\pi*F_c*C)$$

Units:  $R_x$  [Ohm],  $C$  [F],  $F_c$  [Hz]
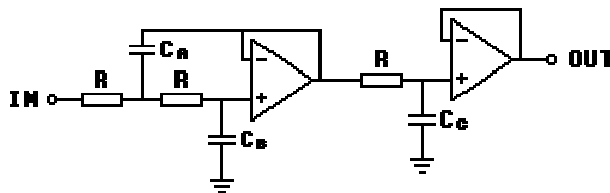
# Active Filter: Bessel (3st order, 18 dB/octave, Lowpass)



$$R=4.7\text{k}-10\text{kOhm}$$


$$C_a=0.9548/(2*\pi*F_c*R)$$

$$C_b=0.4998/(2*\pi*F_c*R)$$

$$C_c=0.7560/(2*\pi*F_c*R)$$

Units:  $R$  [Ohm],  $C_x$  [F],  $F_c$  [Hz]
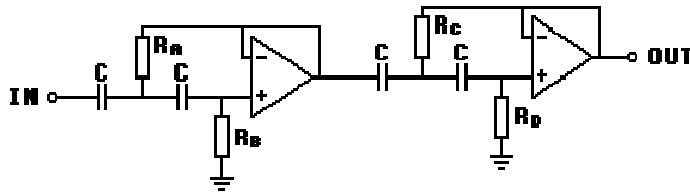
# Active Filter: Bessel (4th order, 24 dB/octave, Highpass)



$$C=4.7\text{n}-10\text{nF}$$

$$R_a=1.3701/(2*\pi*F_c*C)$$


$$R_b=1.4929/(2*\pi*F_c*C)$$

$$R_c=0.9952/(2*\pi*F_c*C)$$

$$R_d=2.5830/(2*\pi*F_c*C)$$

Units:  $R_x$  [Ohm],  $C$  [F],  $F_c$  [Hz]
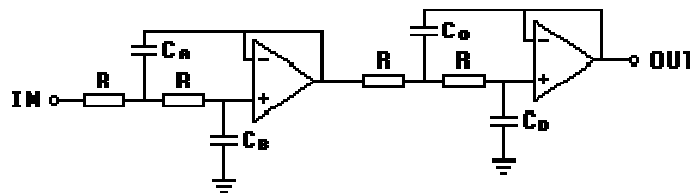
# Active Filter: Bessel (4th order, 24 dB/octave, Lowpass)



$$R=4.7\text{k}-10\text{k}\Omega$$

$$C_a=0.7298/(2*\pi*F_c*R)$$

$$C_b=0.6699/(2*\pi*F_c*R)$$

$$C_c=1.0046/(2*\pi*F_c*R)$$

$$C_d=0.3872/(2*\pi*F_c*R)$$

Units:  $R$  [Ohm],  $C_x$  [F],  $F_c$  [Hz]