

The LED series resistors will need to supply a current of about 7.5mA, so 2.2k should be used. Diodes for the supply should be 1N4004 or equivalent.

If desired, the 12V regulator may be dispensed with, and suitable value resistors placed in series with each relay coil to retain the correct operating voltage. It is the constructor's responsibility to determine the value of these, as the relay current cannot be predicted as there are so many different types available. Use of 15V relays is also possible, if available.

If this arrangement is used, a slight amount of noise may be introduced as the relay operates, because of the sudden application (or removal) of the additional load. It is not expected that this would be a problem in use.

My thanks to Richard for submitting this circuit - it is sure to provide a very high sound quality, and is not overly complex. The active gain control (originally designed by Peter Baxandall) is very effective.

As always, resistors should be 1% metal film types for all signal paths. Their use in the power supply and relay circuits is not necessary, but will not do any harm, either.



Projects Index



Main Index

Copyright Notice. This article, including but not limited to all text and diagrams, is the intellectual property of Richard Crowley and Rod Elliott, and is Copyright (c) 1999. Reproduction or re-publication by any means whatsoever, whether electronic, mechanical or electro-mechanical, is strictly prohibited under International Copyright laws. The author (Richard Crowley) and editor (Rod Elliott) grant the reader the right to use this information for personal use only, and further allow that one (1) copy may be made for reference while constructing the project. Commercial use is prohibited without express written authorisation from Rod Elliott and Richard Crowley.