



+/- 30	18k	0.5 W
+/- 35	22k	0.5 W
+/- 40	25k	0.5 W
+/- 50	33k	0.5 W
+/- 60	39k	0.5 W
+/- 70	47k	1 W
+/- 80	51k	1 W

Table 2 - Resistor Value For 3V Clipping Reference

The table is fairly accurate for a 3V clipping reference, but some amps will not be capable of getting to within 3V of the supply (MOSFET types in particular). In these cases, the resistor value must be calculated.

Current (mA) = Reference Voltage - So a 3V reference requires 3mA [4]

Resistor (k Ohms) = ( ( Supply V - Reference V ) / Current (mA) ) \* 2 [5]

Power (mW) = Current ^ 2 \* Resistor [6]

An example would be an amp with 45V supplies, and requiring a reference voltage of 5V. So ...

From [4] Current = 5mA

From [5] Resistor = ( ( 45 - 5 ) / 5 ) \* 2 = ( 40 / 5 ) \* 2 = 16k Ohms

From [6] Power = 5 ^ 2 \* 16 = 25 \* 16 = 400 mW

Finally, we must select the resistor for the opamp sense inputs. This is required because the voltage on the inverting input must be more positive than that on the non-inverting input for normal operation. The range is quite wide, but not sufficiently so as to cover the entire supply voltage range.

Supply Voltage	Resistance
+/- 20	33k
+/- 30	27k
+/- 35	22k
+/- 40	18k
+/- 50	15k
+/- 60	12k
+/- 70	10k
+/- 80	10k

Table 3 - Opamp Input Resistors

If the correct value is not used for the power supply voltage, the opamp comparator may hold its output high all the time, which will keep the clipping LED turned on. These resistors can be 0.25 Watt for all supply voltages.

### How It Works

Figure 2 shows (in red) the points of the output signal voltage that will trigger the detectors. +ve is the positive power supply voltage and ref+ is the positive reference voltage. The same is applied to the negative supply.

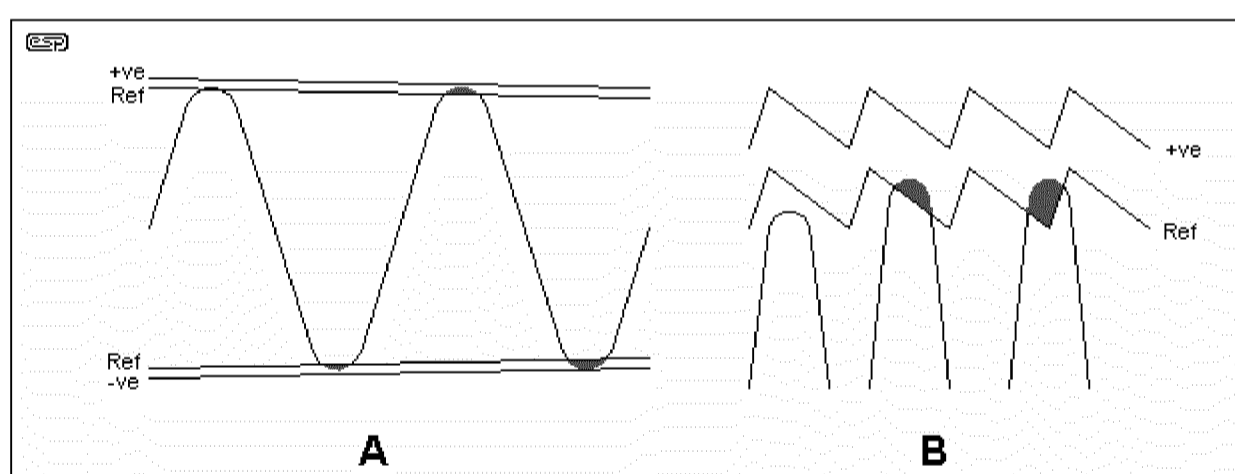


Figure 2 - Instantaneous Voltage Detection

Figure 2A shows the effect as the power supply collapses under sustained load. If the signal drops to a lower level before the supply collapses, the circuit will not be triggered. 2B shows how even the ripple on the power supply is used as a part of the reference, and so will detect that the output signal is about to be clipped based on the supply voltage at any instant in time.

So, as you can see, the actual instantaneous value of the power supply voltage is used as the final reference - the output is measured against this by Q1 and Q2. If the power supply voltage rises or falls, if there is ripple on the supply, this circuit will still indicate if the output of either amp of the stereo pair comes within 3 Volts of the *instantaneous* value of the power supply voltage (or other value - use formulae 4, 5 and 6 to calculate the reference voltage and required resistor values).

U1A operates as a dual comparator - if either transistor stops conducting, the output goes from around 0V to almost the full supply (12V - regulated with a simple zener). This voltage is applied to the inverting input of U1B, and the capacitor is used to "stretch" the pulse so that even momentary clipping will be seen. This opamp drives the clipping LED directly.

By using the input "A", additional separate amplifiers can be connected, so that in a home theatre system, all 5 (or 6) power amps can be monitored, and a single LED will indicate if any amp clips. This can also be done for bi-amped systems.

**Note:** It is vitally important that outputs from amplifiers with separate power supplies are monitored by their own transistor pair - this ensures that each amp is compared to its own power supply (as it should be). *Do not be tempted to try to have one set of detector transistors for multiple separate power supplies.*

Where a common power supply is used for multiple amplifiers (such as in a home theatre system), additional inputs can be added to the detectors - two diodes and a 1k resistor for each amp.

 [Projects Index](#)

 [Main Index](#)

**Copyright Notice.** This article, including but not limited to all text and diagrams, is the intellectual property of Rod Elliott, and is Copyright © 1999. Reproduction or re-publication by any means whatsoever, whether electronic, mechanical or electro-mechanical, is strictly prohibited under International Copyright laws. The author (Rod Elliott) grants the reader the right to use this information for personal use only, and further allows that one (1) copy may be made for reference while constructing the project. Commercial use is prohibited without express written authorisation from Rod Elliott.

Updates: 05 May 05 - changed resistor value to allow more reliable detection at higher temperatures.