

2007. 10. 27. péntek

XVI. Előadás (7. hét)

Múltkor példát folyt... =]

$$f_H = 2,8 \text{ kHz} \quad a_H = -0,89 \text{ dB}$$

$$f_S = 8 \text{ kHz} \quad a_S = -26 \text{ dB}$$

$$\Rightarrow P_1 = -1,2853$$

$$P_2 = -0,64265 + j 1,113$$

$$P_3 = -0,64265 - j 1,113$$

$$F(p) = \frac{1}{B_0 + B_1 p + \dots + B_n p^n} \rightarrow (p - P_3)(p - P_2)(p - P_1) =$$
$$= p^3 + 2,2506 p^2 + 3,304 p + 2,128 = \quad | : 2,28$$
$$= 0,471 p^3 + 1,203 p^2 + 1,5561 p + 1$$

$$F(p) = \frac{1}{B(p)} \rightarrow \Omega_H = 1 \rightarrow j1 \Rightarrow -0,89 \text{ dB}$$

$$\Omega_S = 2,8171 \rightarrow j 2,8171 \Rightarrow -20,8 \text{ dB} \Rightarrow \text{negy, az -26 dB-re!}$$

MATLAB:

$$\gg mp = [1];$$

$$\gg np = \begin{bmatrix} 0,471 & 1,287 & 1,556 & 1 \end{bmatrix};$$

$p^3 \quad p^2 \quad p^1 \quad p^0$

(felvétel) $\gg w = 0.1 : 0,02 : 5;$

(értékelés) $\gg [mag, phase, w] = bode(mp, np, w)$

$$\gg plot(w, mag), grid$$

$$\gg bode(mp, np, w);$$

$$P = \frac{p}{\omega_H}$$

$$F(p) = \frac{1}{0,471 p^3 + 1,287 p^2 + 1,556 p + 1} =$$

$$\frac{1}{\left(\frac{p}{\omega_H}\right)^3 + \left(\frac{p}{\omega_H}\right)^2 + \left(\frac{p}{\omega_H}\right) + 1}$$

$$\omega_H = 2,8 \cdot 2\pi \cdot 10^3 = 19,593 \frac{\text{krad}}{\text{sec}}$$

$$= \frac{1}{8,0498 \cdot 10^{-14} p^3 + 3,9117 \cdot 10^{-2} p^2 + 8,8205 \cdot 10^{-1} p + 1}$$

$$\rightarrow m_p, n_p, k_r \Rightarrow 1000, 1000, 70000 ;$$


$$\text{printsys}(m_p, n_p) \frac{1}{\dots}$$

Megvalósítás

1. fordulatás $P_1 \Rightarrow p_1 = P_1 \cdot \overset{12593}{\omega_H} \Rightarrow -22612$



$P_2 \Rightarrow \Rightarrow -11306 + j 19583$

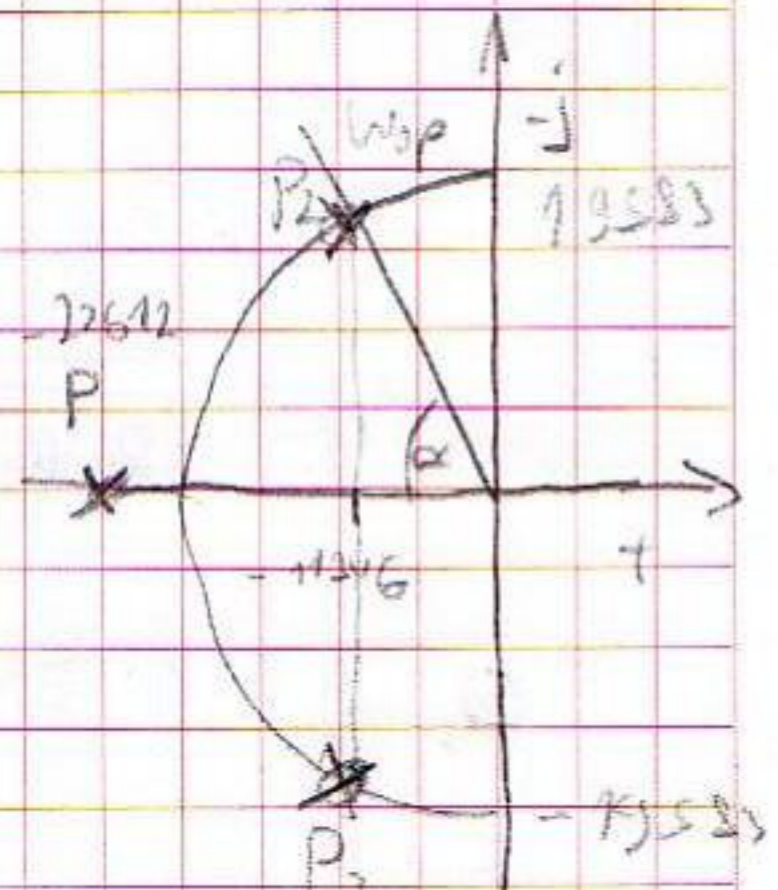2. fordulatás $P_3 \Rightarrow \Rightarrow -11306 - j 19583$ } $\left(\begin{matrix} \Rightarrow \omega_{op} \\ \Rightarrow Q_r \end{matrix} \right)$



Konstrukció

1. fordulatás

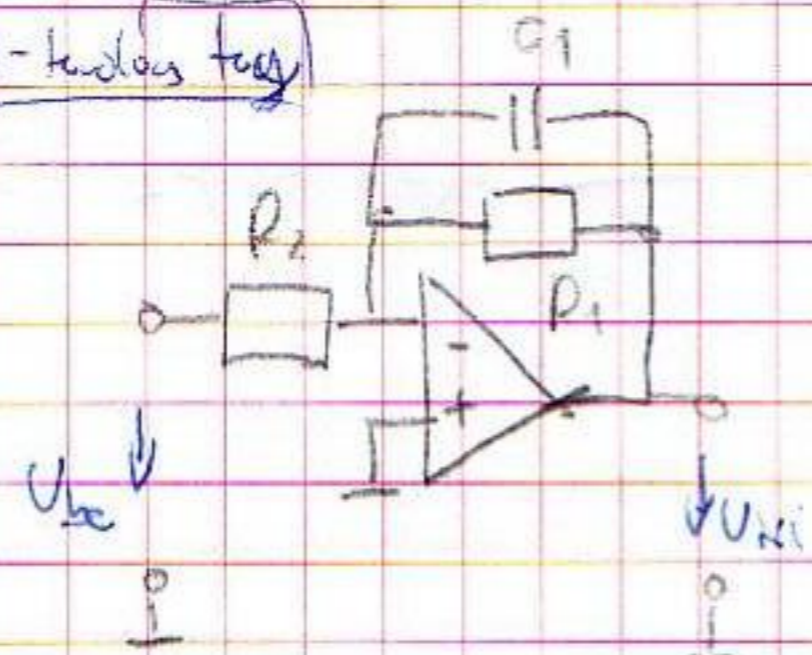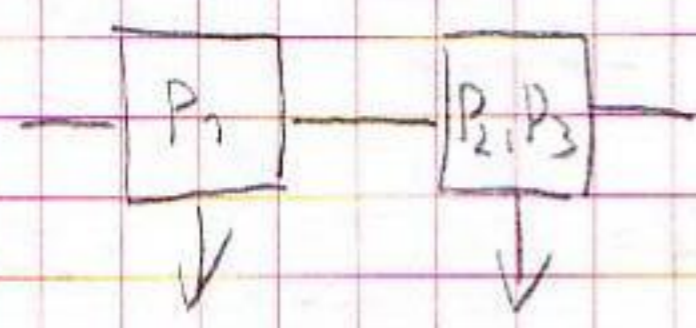

$$\omega_{oe} = \frac{1}{R_1 C_1}$$

$$A_{uo} = -\frac{R_1}{R_2}$$

$$\Rightarrow R_1 = R_2 = R = \frac{1}{\omega_{oe} C_1} = 22,1 \text{ k}\Omega$$


$$A_{uo} = 1 \Rightarrow R_1 = R_2 = R$$

$$\Rightarrow R_1 = 22,1 \text{ k}\Omega, C_1 = 1 \text{ nF}$$

±5%, ±2%, ±1%

↓
időben stabilis juss


2-fordulós tag számítása

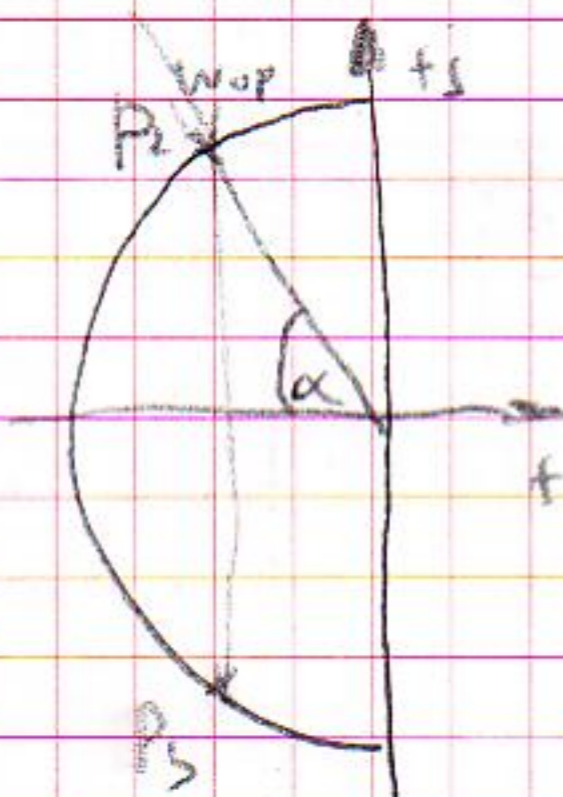

$$\omega_{op} = \sqrt{19583^2 + 11306^2} \Rightarrow 22612 \frac{\text{rad}}{\text{sec}}$$

$$\tan \alpha = \frac{19583}{11306} = \sqrt{3} \Rightarrow \alpha = 60^\circ$$
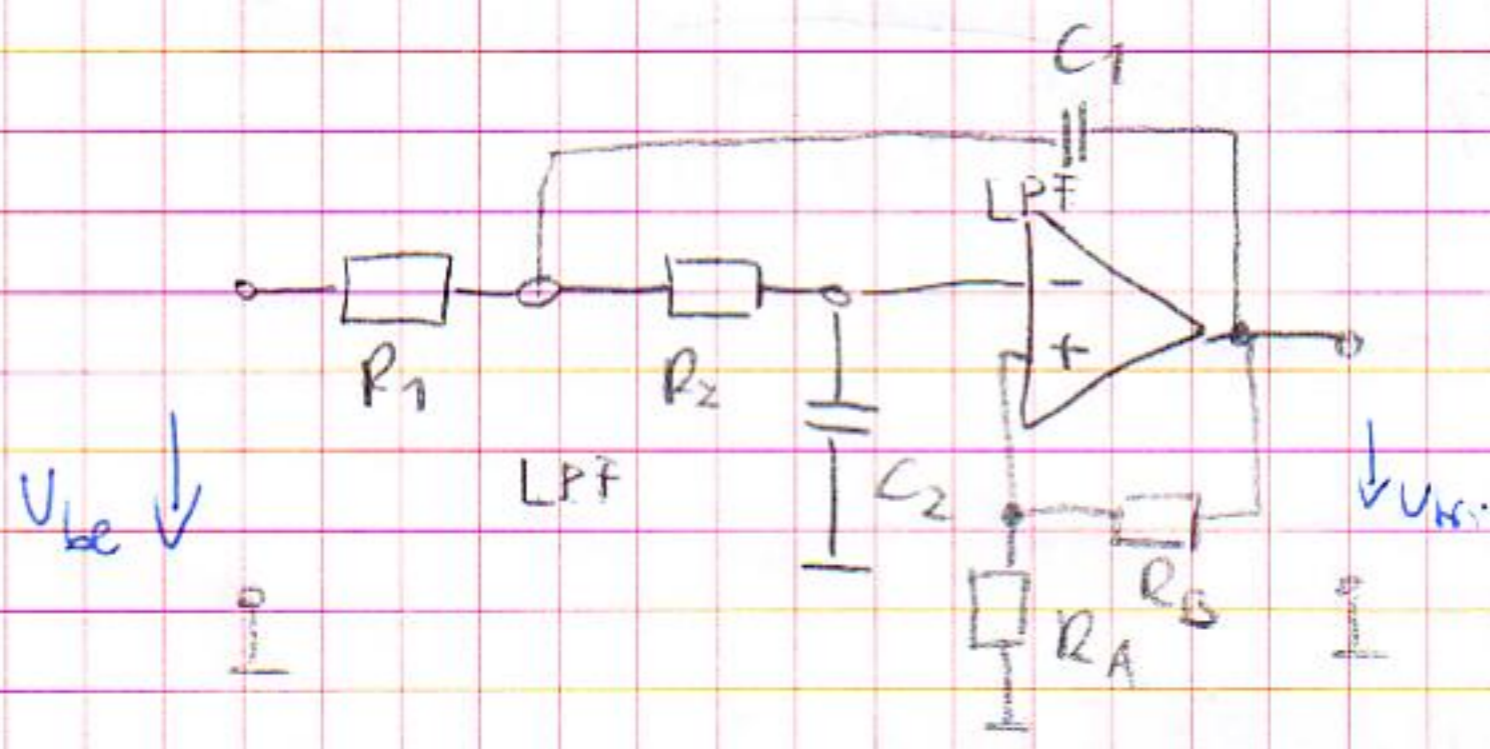
$$Q_p = \frac{1}{2 \cos \alpha} \Rightarrow \frac{1}{2 \cdot 0,5} = 1$$



$$A_{uo} = K = 1$$

$$A_{uo} = K = 1$$

$$\omega_{po} = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \Rightarrow \omega_0 = \frac{1}{R \sqrt{C_1 C_2}} \Rightarrow R \sqrt{C_1 C_2} = \frac{1}{\omega_{op} R}$$

$$Q_p \omega_{op} = \frac{1}{R_1 C_1 (1-K) + (R_1 + R_2) C_2}$$

$$C_1 C_2 = \left(\frac{1}{\omega_{op} R}\right)^2 \Rightarrow C_1 = \frac{1}{(22612 \cdot 20)^2} = 1 \text{ nF}$$

$$Q_p = 1$$

$$\omega_{op} = 22612$$

$$R_1 = R_2 = R$$


$$\Rightarrow \frac{1}{\omega_{op}} = (R_1 + R_2) C_2 \Rightarrow C_2 = \frac{1}{2R \omega_{op}} = 1 \text{ nF} \Rightarrow$$

$$R = \frac{1}{2 \cdot 10^{-9} \cdot 22612} \approx 20 \text{ k}\Omega$$


22,1k

$C_2 = 1 \text{ nF} \Rightarrow R = 22,1 \text{ k}\Omega \Rightarrow C_1 = 1 \text{ nF}$

vágsó megold \Rightarrow

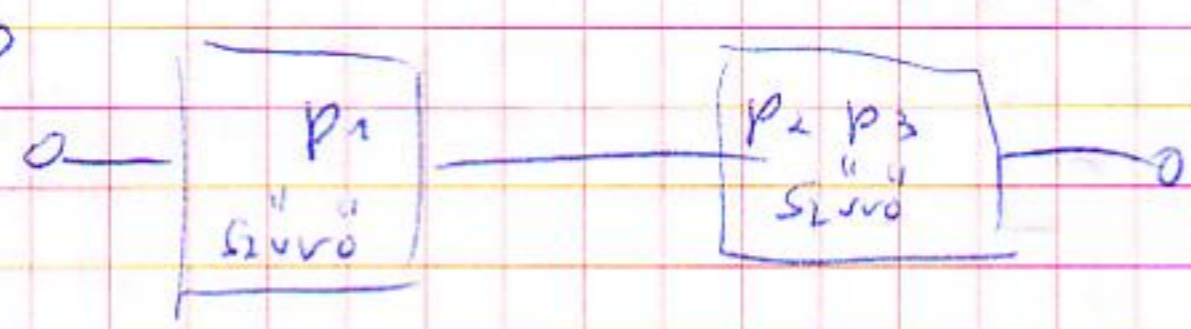


FUU, DENEM SEKRÉTJUN
A TEVERCSET (L)

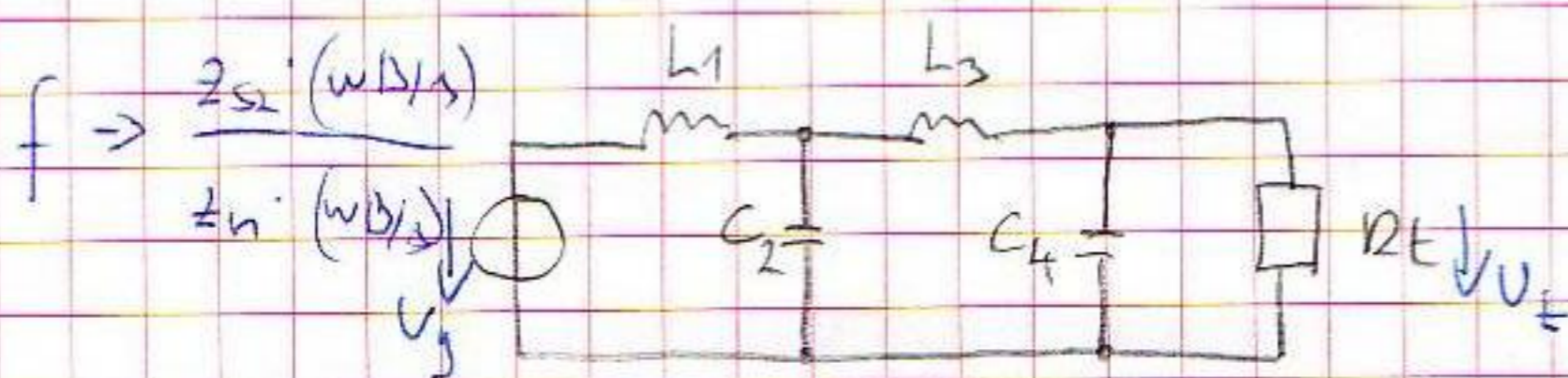


Betűjel	jelkép	$Z(s)$	$Z(s) \cdot wB/s$	echív
L		sL	$sL \cdot \frac{wB}{s} \Rightarrow wB L$	$R^* = wB L$
R		R	$R \cdot \frac{wB}{s} = \frac{1}{s} \frac{wB}{R}$	$C^* = \frac{wB}{R}$
C		$\frac{1}{sC}$	$\frac{1}{sC} \cdot \frac{wB}{s} = \frac{1}{s^2} \frac{wB}{C}$	D^*

Konverter technika

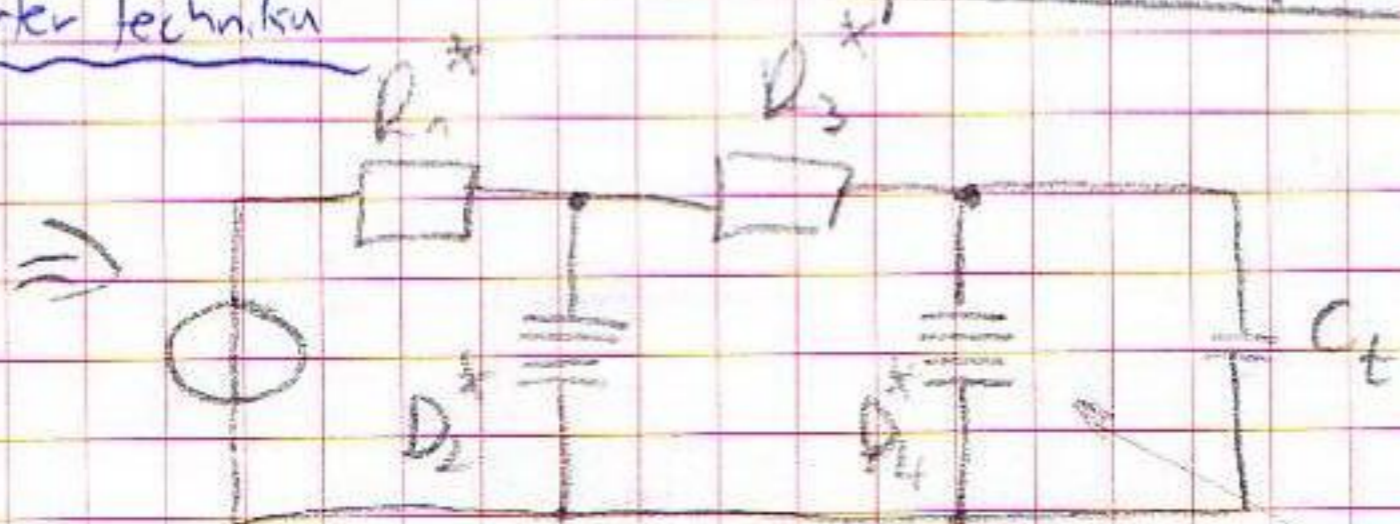

doppa kondi LOL =]

G.I.C. (general impedance converter)


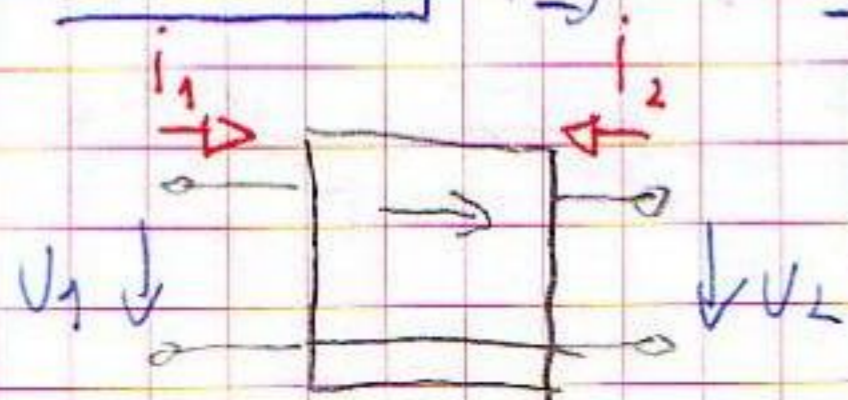


$$U_1 = U_2 \Rightarrow U_1 = h_{11} i_1 + h_{12} U_2$$

$$i_2 = -h(s) i_1 \Rightarrow i_2 = h_{21} i_1 + h_{22} U_2$$

$$U_1 = U_2$$

$$i_2 = -h(s) \cdot i_1$$

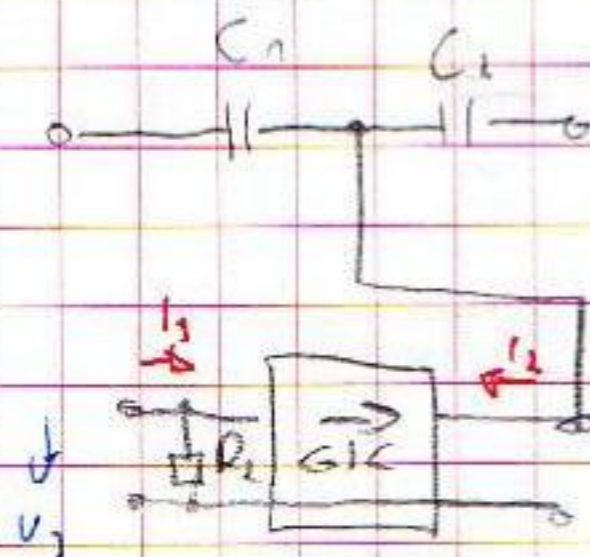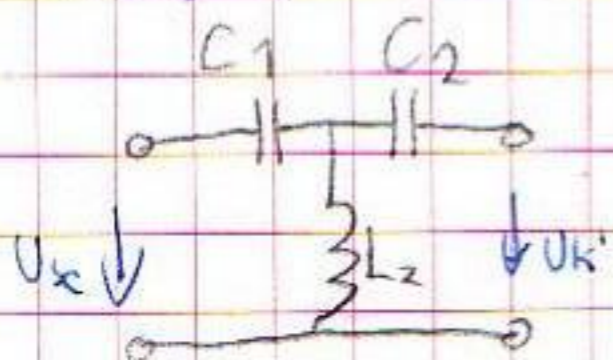


$$U_1 = U_2$$

$$i_1 = -\frac{U_1}{R_2} = -\frac{U_2}{R_2}$$

$$i_2 = +h(s) \cdot \frac{U_2}{R_2}$$

$$\Rightarrow \frac{U_2}{i_2} = \frac{R_2}{h(s)} \Rightarrow \frac{R}{wB} = \frac{R_2}{wB} \Rightarrow R = R_2$$

fordítva

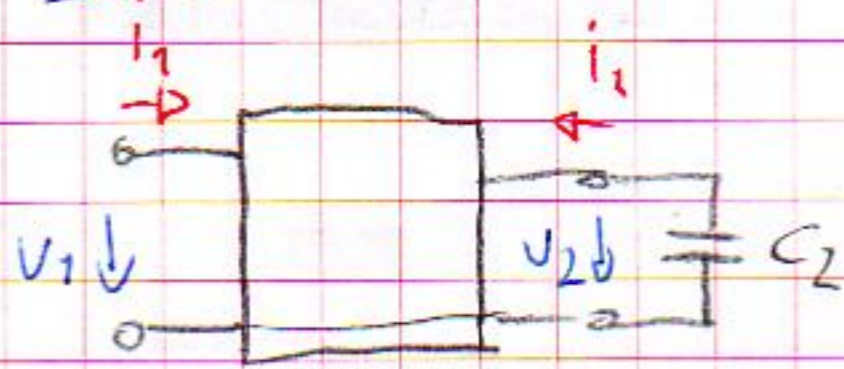


$$U_1 = U_2$$

$$i_2 = -h(s) \cdot i_1 \Rightarrow \frac{U_1}{i_1} = Z_{be} = \frac{U_2}{i_2} = -\frac{U_2}{i_2} = h(s) = \frac{U_2}{i_2} \cdot h(s) = Z_2 \cdot h(s) = Z_2 \cdot \frac{\omega_B}{s}$$

$$\Rightarrow i_1 = -\frac{i_2}{h(s)}$$


$$\Rightarrow \frac{1}{s C_2} \cdot \frac{\omega_B}{s} = \frac{1}{s^2} \frac{\omega_B}{C_2} = \frac{1}{D^*}$$

potenciál független:

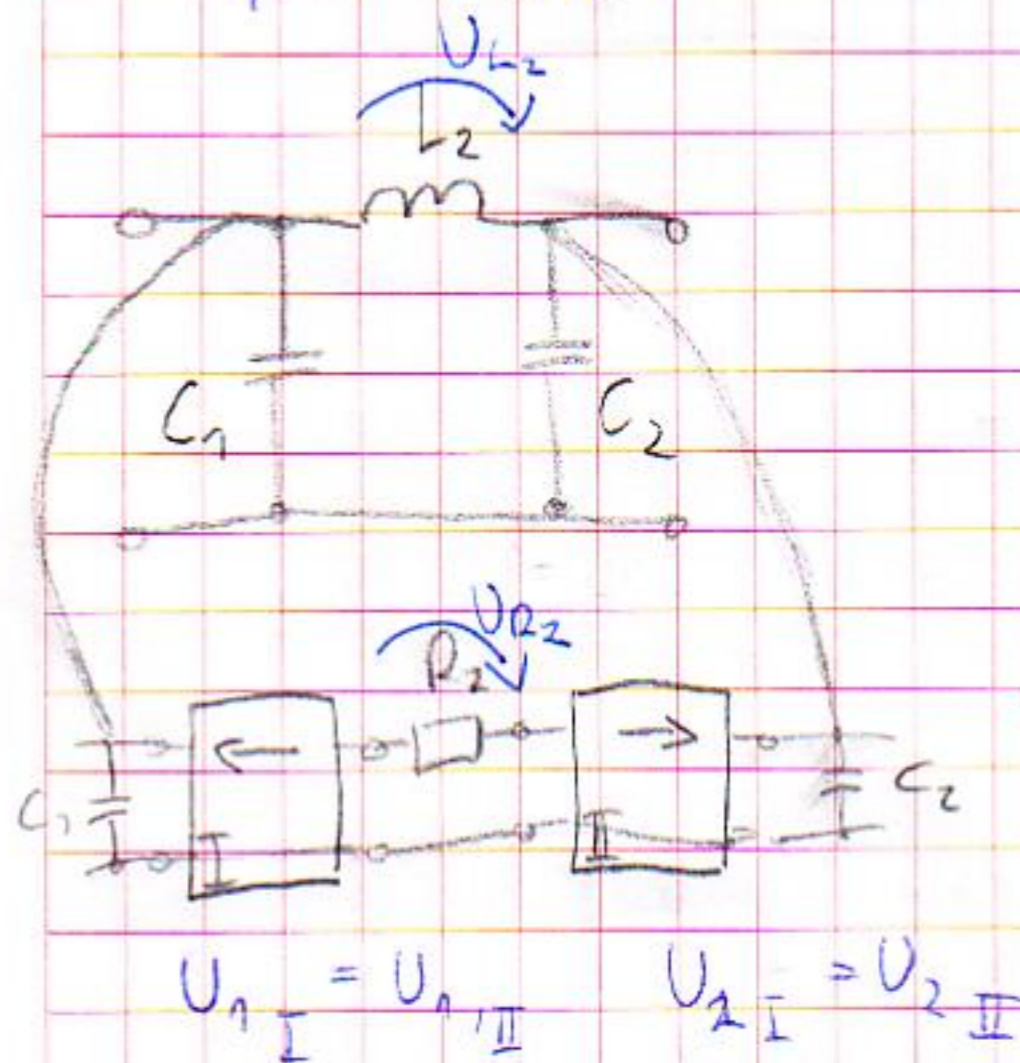

$$U_1 = U_2$$

$$U_{L2} = U_{R2}$$

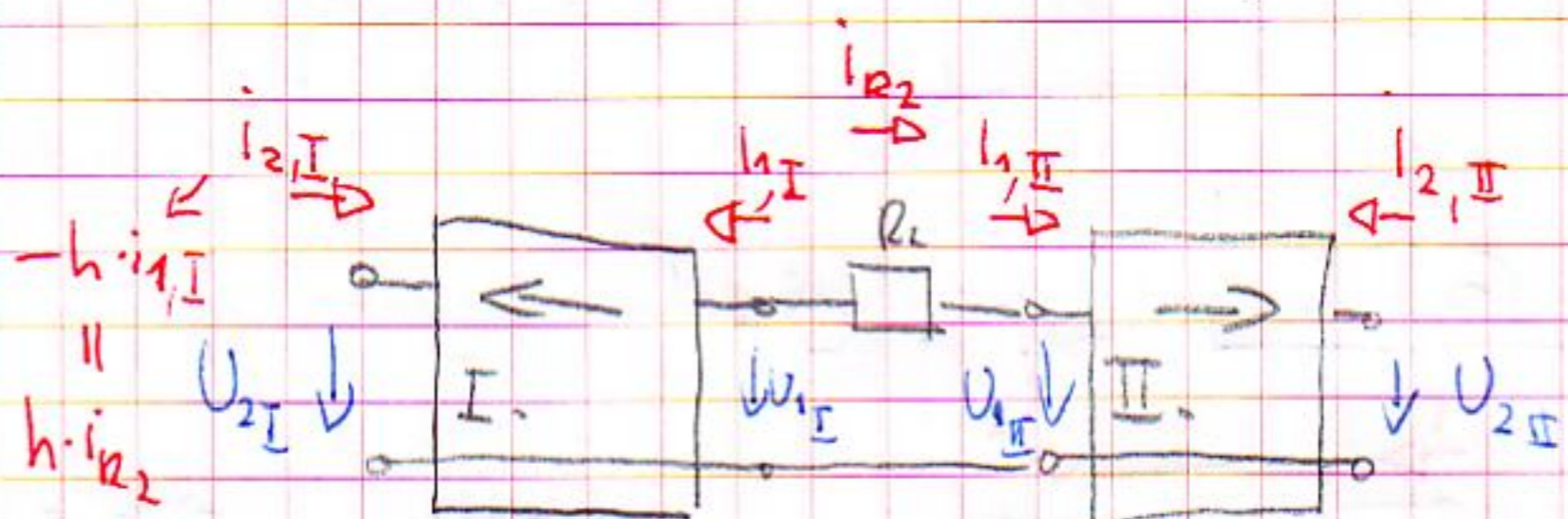


$$U_{1I} = U_{1II} \quad U_{2I} = U_{2II}$$

$$i_{R2} = \frac{U_{R2}}{R_2}$$


$$i_{1I} = -i_{1II} \quad ; \quad i_{1II} = +i_{R2}$$

$$h \frac{U_{L2}}{R_2} \Rightarrow \frac{U_{L2}}{R_2} \cdot \frac{\omega_B}{s}$$

$$\frac{U_{L2}}{i_{L2}} = \frac{U_{L2}}{\frac{U_{L2}}{R_2} \cdot \frac{\omega_B}{s}} = s \cdot \frac{R_2}{\omega_B}$$

GIC-rel szuperkapacitás is létrehozható 

GIC negatívátvételű műveleti erősítővel

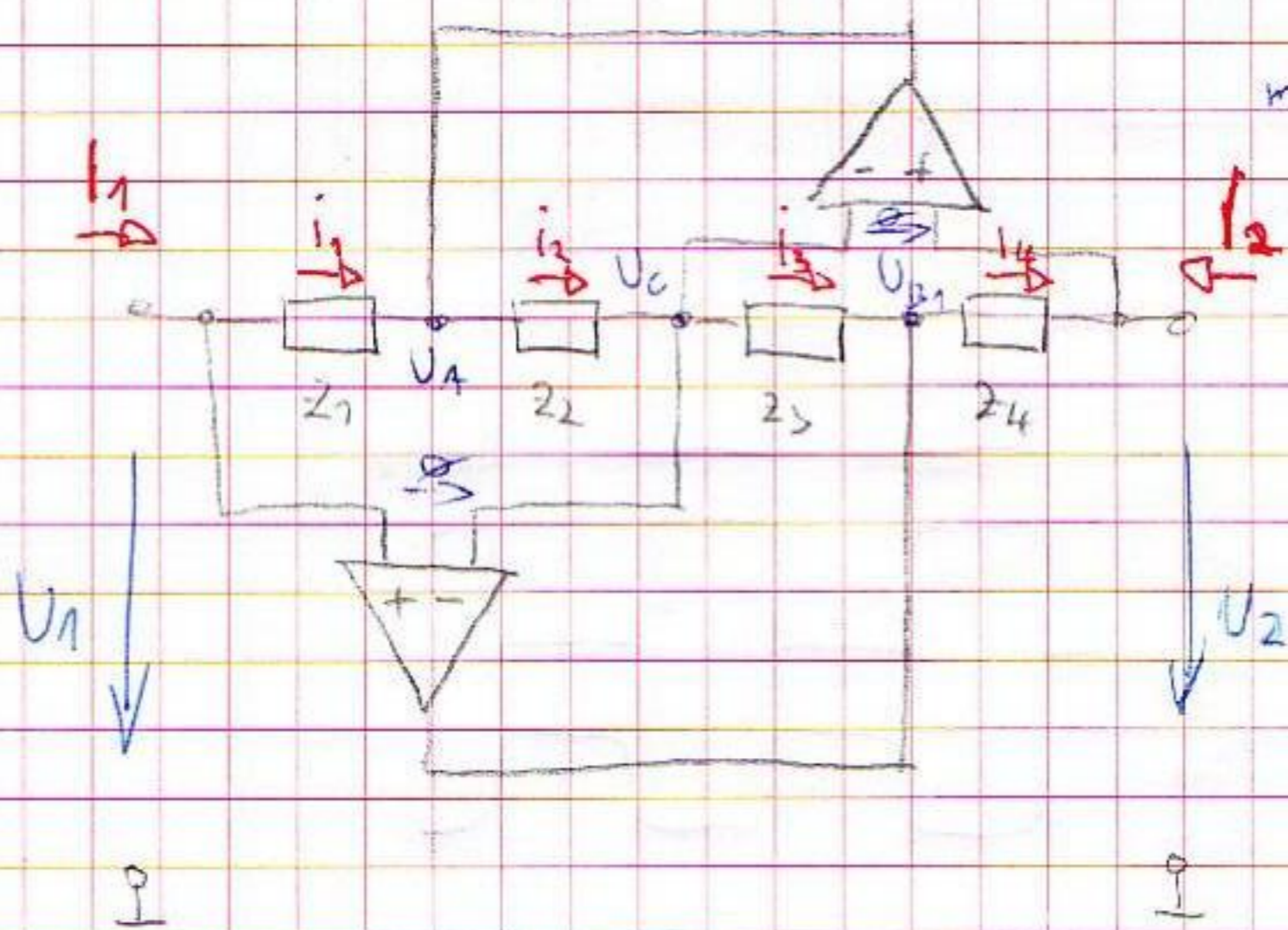

me. $\Rightarrow U^+ - U^- = 0 \Rightarrow U_1 = U_2$

$i_1 \cdot Z_1 + i_2 \cdot Z_2 = 0$

$i_3 \cdot Z_3 + i_4 \cdot Z_4 = 0$

me $i_2 = i_3 = i$

$$\Rightarrow \left. \begin{aligned} i_1 \cdot Z_1 + i \cdot Z_2 &= 0 & \Rightarrow & i_1 \cdot \frac{Z_1}{Z_2} + i = 0 & \Rightarrow & i = -i_1 \cdot \frac{Z_1}{Z_2} \\ i \cdot Z_3 + i_4 \cdot Z_4 &= 0 & \Rightarrow & i + i_4 \cdot \frac{Z_4}{Z_3} = 0 & \Rightarrow & i = -i_4 \cdot \frac{Z_4}{Z_3} \end{aligned} \right\} \Rightarrow$$

$$\Rightarrow i_1 \cdot \frac{Z_1}{Z_2} = i_4 \cdot \frac{Z_4}{Z_3} \quad \left(\begin{array}{l} i_1 = i_1 \\ i_2 = -i_4 \end{array} \right)$$

$$\Rightarrow i_4 \cdot \frac{Z_4 \cdot Z_2}{Z_3 \cdot Z_1} = i_1 \quad i_2 = -i_1 \cdot \frac{Z_4 \cdot Z_2}{Z_3 \cdot Z_1} = h(s)$$