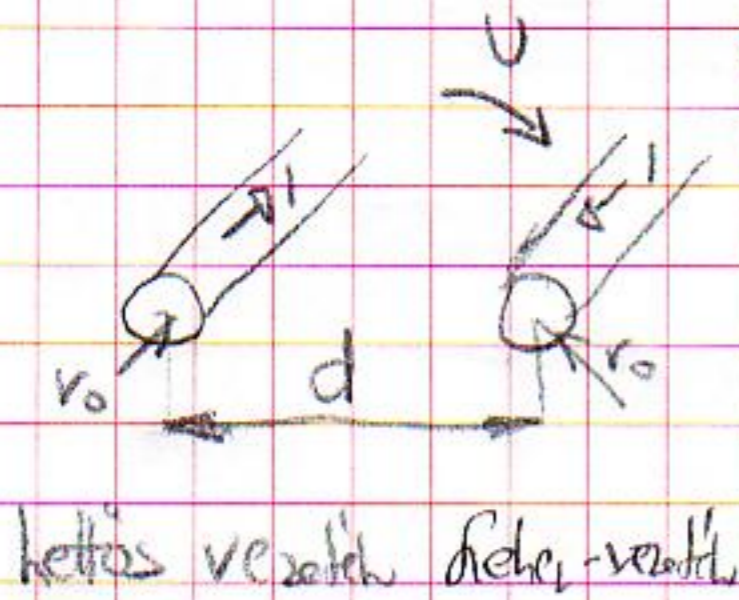


2007.03.28. szerda

XI. Előadás (7. hét)


Távvezetékek



kettes vezeték felcsatolva




$\phi = 0$
amperohallás

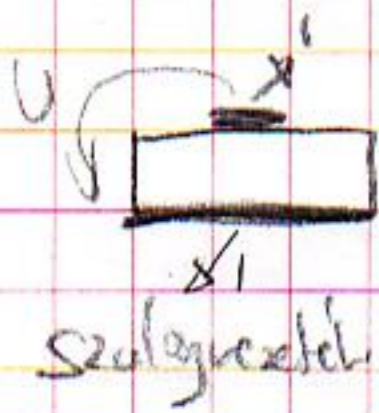

szériavezeték



komplexívus vezeték

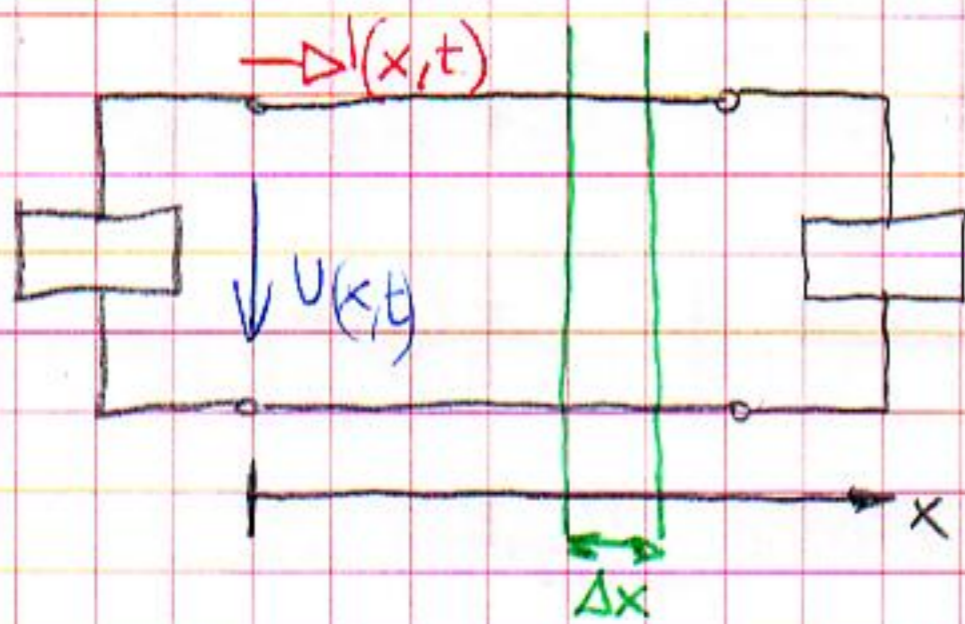


$\frac{dx}{dx}$

$$\oint \vec{E} d\vec{l} = -\frac{\partial}{\partial t} \int \vec{E} d\vec{a}$$

$$\oint \vec{H} d\vec{l} = \int \left(\vec{J} + \frac{\partial \vec{D}}{\partial t} \right) d\vec{a}$$

függetlenség egyenlet

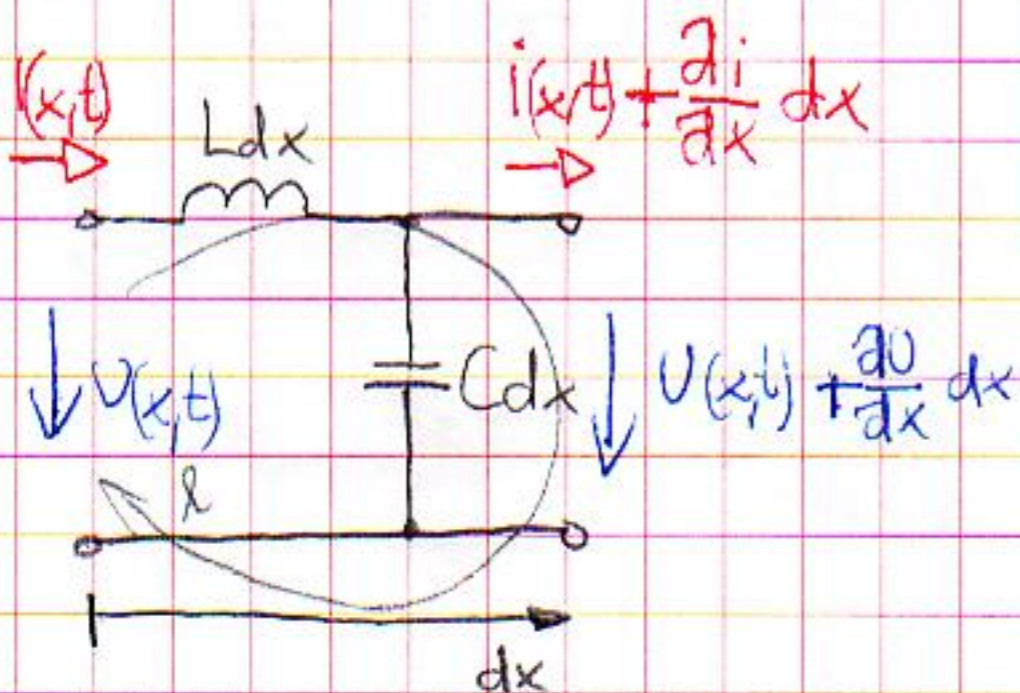

$$q = C dx u(x,t)$$

$$-\frac{dq}{dt} = -C dx \frac{\partial u(x,t)}{\partial t} = i(x,t) dx - i(x,t) dx$$

$$u(x,t) + \frac{\partial u}{\partial x} dx - u(x,t) = -\frac{\partial q}{\partial t} = -\frac{\partial}{\partial t} L dx i(x,t) = -L dx \frac{di}{dt}$$

$$\boxed{-\frac{\partial u(x,t)}{\partial x} = L \frac{di(x,t)}{\partial t}}$$

$$\boxed{-\frac{\partial i(x,t)}{\partial x} = C \frac{\partial u(x,t)}{\partial t}}$$

$$\boxed{-\frac{\partial^2 u}{\partial x^2} = L \frac{\partial di}{\partial t dx} = -LC \frac{\partial^2 u}{\partial t^2}}$$

$$\boxed{\frac{\partial^2 i(x,t)}{\partial x^2} = LC \frac{\partial^2 i(x,t)}{\partial t^2}}$$

1D hullámegyenlet megoldása $f\left(t \mp \frac{x}{v}\right)$ haladó hullám $\pm x$


$$t \mp \frac{x}{v} = \alpha$$

$$\left. \begin{aligned} \frac{\partial f(\alpha)}{\partial x} &= \frac{\partial f}{\partial \alpha} \cdot \frac{\partial \alpha}{\partial x} = \frac{\partial f}{\partial \alpha} \left(\mp \frac{1}{v}\right) \\ \frac{\partial f(\alpha)}{\partial t} &= \frac{\partial f}{\partial \alpha} \cdot \frac{\partial \alpha}{\partial t} = \frac{\partial f(\alpha)}{\partial \alpha} \end{aligned} \right\} \begin{aligned} \frac{\partial f}{\partial x} &= \mp \frac{1}{v} \frac{\partial f}{\partial t} \\ \frac{\partial^2 f}{\partial x^2} &= + \frac{1}{v^2} \frac{\partial^2 f}{\partial t^2} \end{aligned}$$

$$\frac{1}{v^2} = LC = \mu \epsilon \quad v = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\mu \epsilon}} = \frac{1}{\sqrt{\epsilon_0 \mu_0}} \quad \frac{1}{\sqrt{\epsilon_r \mu_r}} = \frac{c_0}{\sqrt{\epsilon_r \mu_r}}$$

hullám impedanciája $Z_0 = \frac{U^+}{I^+} = \sqrt{\frac{L}{C}}$

Vesztéses ábrázolás

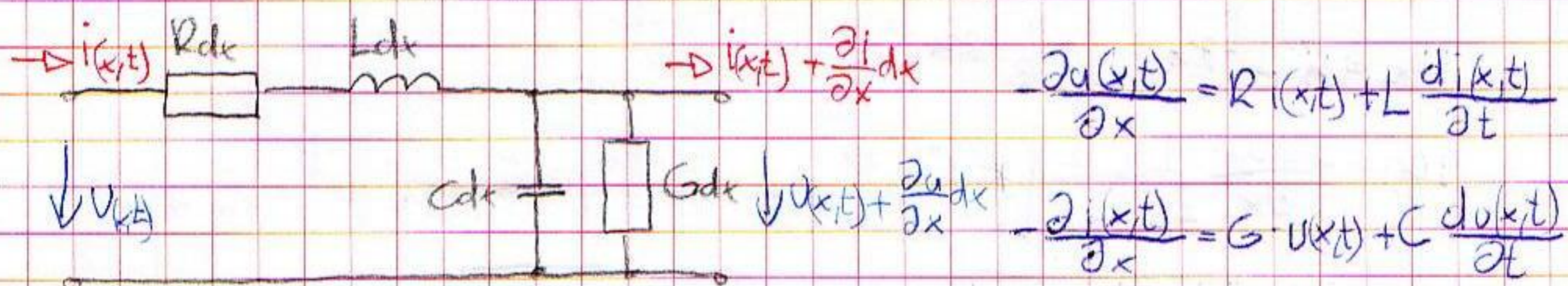

$$-\frac{\partial^2 u}{\partial x^2} = -R \left(Gu + C \frac{\partial u}{\partial t} \right) - L \left(G \frac{\partial u}{\partial t} + C \frac{\partial^2 u}{\partial t^2} \right)$$

$$\frac{\partial^2 u}{\partial x^2} = LC \frac{\partial^2 u}{\partial t^2} + (RC + LG) \frac{\partial u}{\partial t} + RG u$$

Ha $R=0, G=0$ $\frac{\partial^2 u}{\partial x^2} = LC \frac{\partial^2 u}{\partial t^2}$

Ha $\frac{R}{L} = \frac{G}{C}$ torzításmentes hullámterjedés (THOMSON-FÉLE)

$$u^+(x,t) = U_0^+ e^{-\alpha x} f\left(t - \frac{x}{v}\right) \rightarrow$$

$$u^-(x,t) = U_0^- e^{\alpha x} f\left(t + \frac{x}{v}\right) \leftarrow$$

$$-\frac{\partial u}{\partial x} = Ri + L \frac{\partial i}{\partial t}$$

$$\frac{\partial i}{\partial x} = Gu + C \frac{\partial u}{\partial t}$$

Szinuszos gerj

$$i(x,t) = \operatorname{Re}\{I(x) e^{j\omega t}\}$$

$$u(x,t) = \operatorname{Re}\{U(x) e^{j\omega t}\}$$

$$-\frac{\partial U(x)}{\partial x} = R I(x) + j\omega L I(x) = (R + j\omega L) I(x) = Z_s(j\omega) I(x)$$

$$-\frac{\partial I(x)}{\partial x} = G U(x) + j\omega C U(x) = (G + j\omega C) U(x) = Y_p(j\omega) U(x)$$

$$\frac{\partial^2 U(x)}{\partial x^2} = Z_s Y_p U(x) = \gamma^2 U(x)$$

$$U(x) = U_0^+ e^{-\gamma x} + U_0^- e^{+\gamma x}$$

$$I(x) = -\frac{\partial U(x)}{\partial x} \frac{1}{Z_s} = \frac{1}{Z_s} (\gamma U_0^+ e^{-\gamma x} - \gamma U_0^- e^{+\gamma x}) = \frac{\gamma}{Z_s} (U_0^+ e^{-jx} - U_0^- e^{+jx})$$

$$\frac{1}{Z_0} = \frac{\gamma}{Z_s} = \frac{\sqrt{Z_s Y_p}}{Z_s} = \sqrt{\frac{Y_p}{Z_s}} \Rightarrow Z_0 = \sqrt{\frac{Z_s}{Y_p}} = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \quad \text{HULLÁMIMPEDANCIA}$$

$$I_0^+ e^{-jx} + I_0^- e^{+jx} = \frac{U_0^+}{Z_0} e^{-jx} - \frac{U_0^-}{Z_0} e^{+jx}$$

$$I_0^+ = \frac{U_0^+}{Z_0}$$

$$I_0^- = -\frac{U_0^-}{Z_0}$$

$$\Rightarrow Z_0 \triangleq \frac{U_0^+}{I_0^+} = -\frac{U_0^-}{I_0^-}$$

Amplifikációs értéke


$$\gamma = \sqrt{Z_s Y_p} = \sqrt{(R + j\omega L)(G + j\omega C)} = \alpha + j\beta \quad \text{TERJEDESI EGYÜTHATÓ}$$

$$U^+(x) = U_0^+ e^{-\gamma x} = U_0^+ e^{-(\alpha + j\beta)x} = U_0^+ e^{-\alpha x} e^{-j\beta x}$$


$$u^+(x,t) = \operatorname{Re}\{U_0^+ e^{-\alpha x} e^{-j\beta x} e^{j\omega t}\} = \operatorname{Re}\{U_0^+ e^{-\alpha x} e^{j(\omega t - \beta x)}\}$$

csillapított hullám fázis sebessége
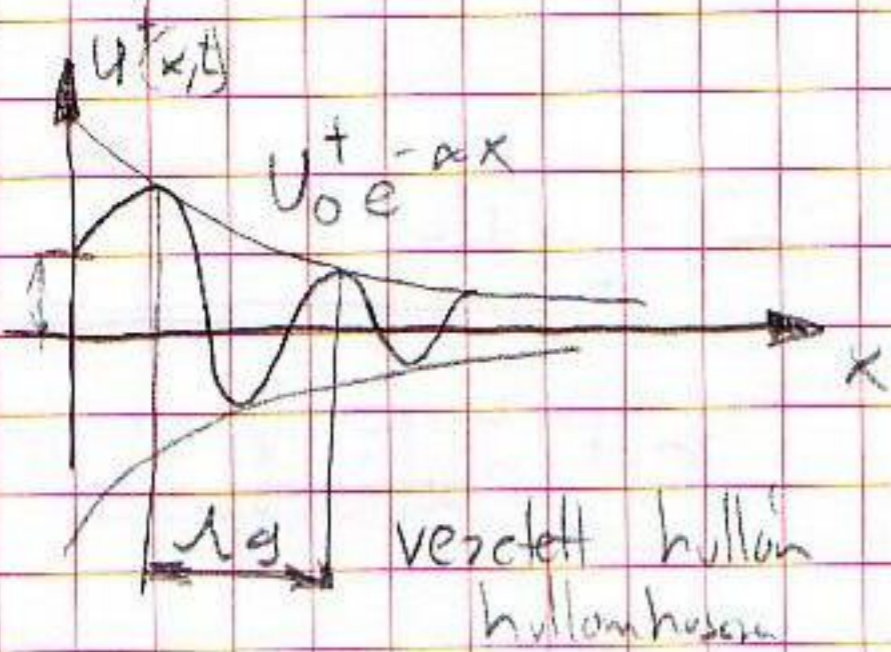
$$u^+(x,t) = U_0^+ e^{-\alpha x} \cos(\omega t - \beta x)$$


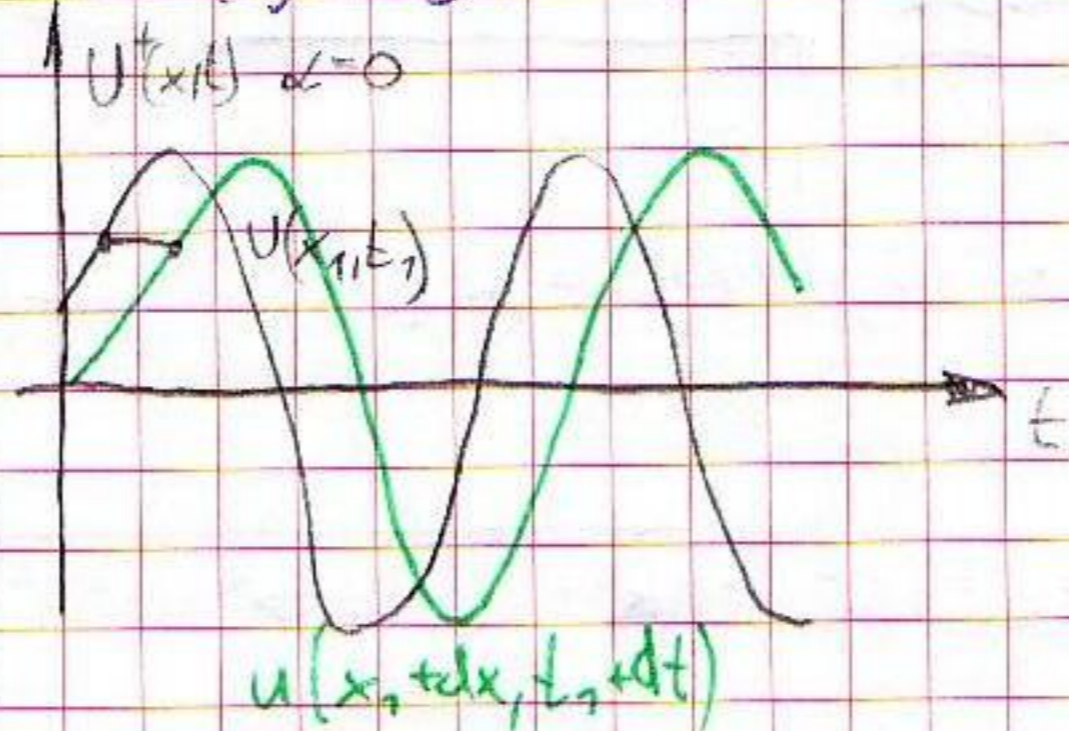
$$U^+(x) = U_0^+ e^{-\alpha x} e^{j\omega(t - \frac{x}{v_f})} \quad v_f = \frac{\omega}{\beta}$$




$$U_0^+ e^{-j(\omega t_1 - \beta x_1)} = U_0^+ e^{-j(\omega(t_1 + dt) - \beta(x_1 + dx))}$$

$$-(\omega t_1 - \beta x_1) = -[\omega(t_1 + dt) - \beta(x_1 + dx)] \Rightarrow \omega dt - \beta dx = 0$$

$$\frac{dx}{dt} = \frac{\omega}{\beta} = v_f$$

(ideális húrvez) $\gamma = \alpha + j\beta$
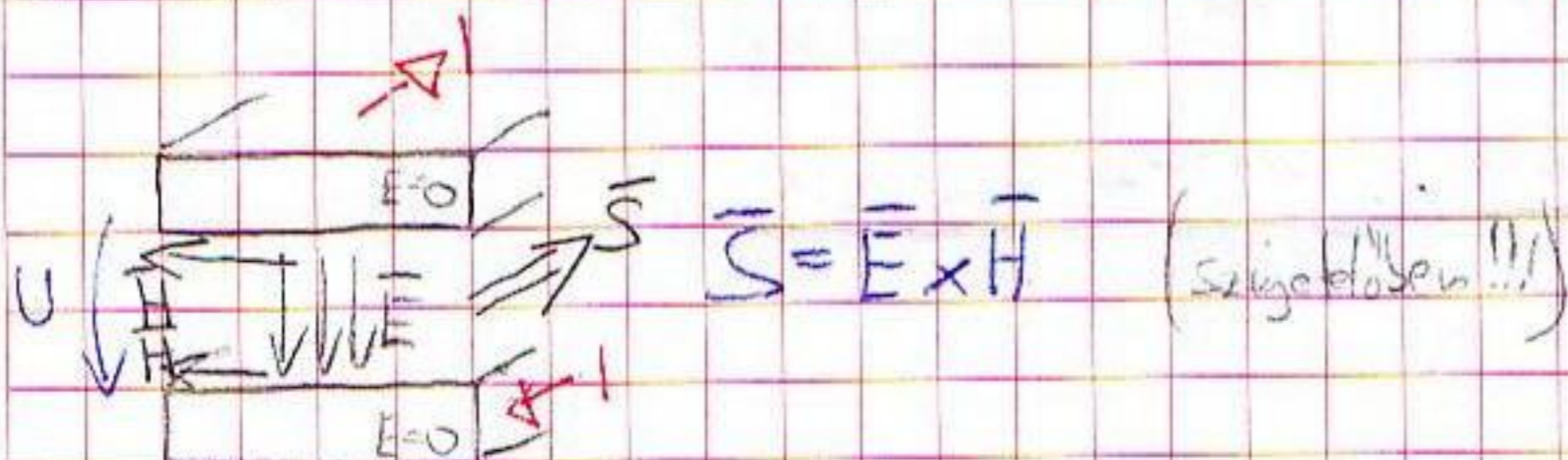
$$\begin{matrix} R=0 \\ G=0 \end{matrix} \Rightarrow \gamma = \sqrt{j\omega L + j\omega C} = j\omega \sqrt{LC} = j\beta$$



$$U_0^+ e^{-j(\omega t - \beta(x+d))} = U_0^+ e^{-j(\omega t - \beta x \pm 2\pi)}$$

$$\beta \lambda_g = 2\pi \Rightarrow \lambda_g = \frac{2\pi}{\beta} \neq \lambda \quad \text{Dobozkér. hullám}$$

$$V(x,t) = U_0^+ e^{-\alpha x} e^{j\omega(t - \frac{x}{v_f})} + U_0^- e^{+\alpha x} e^{j\omega(t + \frac{x}{v_f})}$$

$$I(x,t) = \frac{U_0^+}{Z_0} e^{-\alpha x} e^{j\omega(t - \frac{x}{v_f})} + \frac{U_0^-}{Z_0} e^{+\alpha x} e^{j\omega(t + \frac{x}{v_f})}$$

$$u(x,t) = U_0^+ e^{-\alpha x} \cos(\omega t - \beta x) + U_0^- e^{+\alpha x} \cos(\omega t + \beta x)$$

$$i(x,t) = \frac{U_0^+}{Z_0} e^{-\alpha x} \cos(\omega t - \beta x) + \frac{U_0^-}{Z_0} e^{+\alpha x} \cos(\omega t + \beta x)$$

$$\alpha = ? \quad \beta = ?$$

$$\gamma = \sqrt{Z_s Y_p} = \sqrt{(R + j\omega L)(G + j\omega C)} = \alpha + j\beta$$

$$\gamma^2 = \alpha^2 + 2j\alpha\beta - \beta^2 = (R + j\omega L)(G + j\omega C) = RG - \omega^2 LC + j\omega(RC + GL)$$

$$\text{Re: } \alpha^2 - \beta^2 = RG - \omega^2 LC$$

$$|\gamma| = \alpha^2 + \beta^2 = \sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)}$$

$$- \left. \beta = \frac{1}{\sqrt{2}} \sqrt{\omega^2 LC - RG + \sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)}} \right\}$$

$$+ \left. \alpha = \frac{1}{\sqrt{2}} \sqrt{RG - \omega^2 LC + \sqrt{(R^2 + \omega^2 L^2)(G^2 + \omega^2 C^2)}} \right\}$$

$$\text{hu } \omega \rightarrow \infty \Rightarrow \alpha \rightarrow 0$$

Fázis sebesség, csoport sebesség:

$$\omega_1, \omega_2 \quad \beta_1, \beta_2$$

$$\cos \alpha + \cos \beta = 2 \cos \frac{\alpha + \beta}{2} \cos \frac{\alpha - \beta}{2}$$

$$U(x, t) = U_0 \left[\cos(\underbrace{\omega_1 t - \beta_1 x}_\alpha) + \cos(\underbrace{\omega_2 t - \beta_2 x}_\beta) \right]$$

$$= 2U_0 \cos \frac{(\omega_1 + \omega_2)t - (\beta_1 + \beta_2)x}{2} \cos \frac{(\omega_1 - \omega_2)t - (\beta_1 - \beta_2)x}{2}$$

