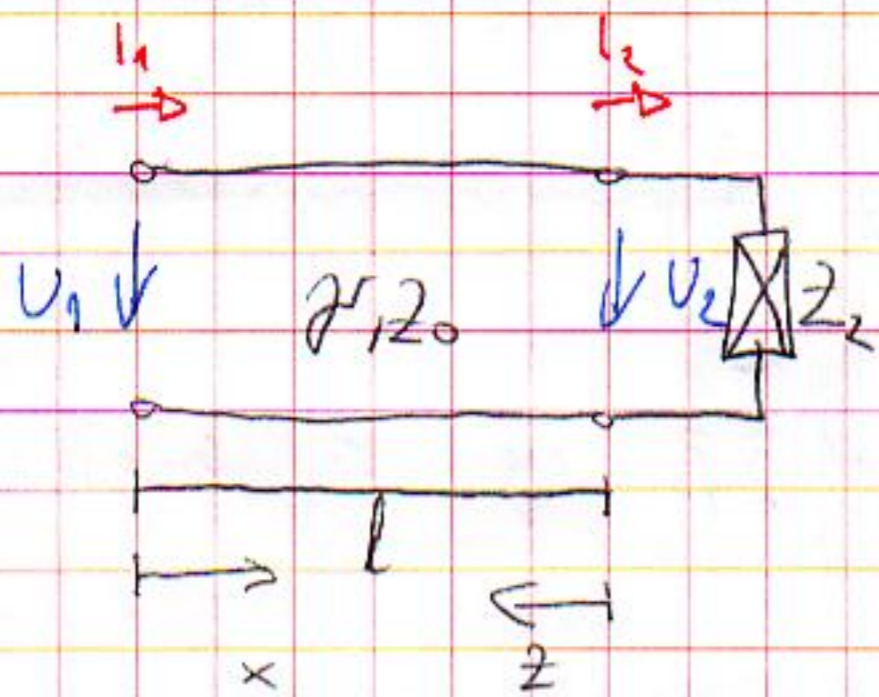


2007. 04. 10. kedd

XIII. előadás (9. hét)

Távvezeték (folyt.)

Távvezeték, mint kétkapú:



$$U_1 = U_2 \operatorname{ch} \gamma l + I_2 Z_0 \operatorname{sh} \gamma l$$

$$I_1 = \frac{U_2}{Z_0} \operatorname{sh} \gamma l + I_2 \operatorname{ch} \gamma l$$

$$Z_{\text{be}} = Z_0 \frac{Z_2 \operatorname{ch} \gamma l + Z_0 \operatorname{sh} \gamma l}{Z_0 \operatorname{ch} \gamma l + Z_2 \operatorname{sh} \gamma l}$$

$$\underline{P} = \underline{A} \underline{S}, \quad \begin{bmatrix} U_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} \operatorname{ch} \gamma l & Z_0 \operatorname{sh} \gamma l \\ \frac{\operatorname{sh} \gamma l}{Z_0} & \operatorname{ch} \gamma l \end{bmatrix} \begin{bmatrix} U_2 \\ I_2 \end{bmatrix}$$

$$\det(A) = \operatorname{ch}^2 \gamma l - \operatorname{sh}^2 \gamma l = 1$$

\Rightarrow reciprokus

$$A_{11} = A_{22} \Rightarrow \text{szimmetrikus}$$

$$\underline{Z}, \quad \begin{bmatrix} U_1 \\ U_2 \end{bmatrix} = \underline{Z} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$U_2 = \frac{Z_0}{\operatorname{sh} \gamma l} (I_1 - I_2 \operatorname{ch} \gamma l)$$


$$U_1 = \frac{Z_0}{\operatorname{sh} \gamma l} (I_1 \operatorname{ch} \gamma l - I_2 \operatorname{ch}^2 \gamma l) + I_2 \frac{Z_0 \operatorname{sh} \gamma l^2}{\operatorname{sh} \gamma l}$$

$$\begin{bmatrix} U_1 \\ U_2 \end{bmatrix} = \frac{Z_0}{\operatorname{sh} \gamma l} \begin{bmatrix} \operatorname{ch} \gamma l & -1 \\ 1 & -\operatorname{ch} \gamma l \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$Z_{12} = -Z_{21} \Rightarrow \text{reciprok}$$

$$Z_{11} = -Z_{22} \Rightarrow \text{szimmetrikus}$$


$\Rightarrow \exists T, \Pi$ -helykép

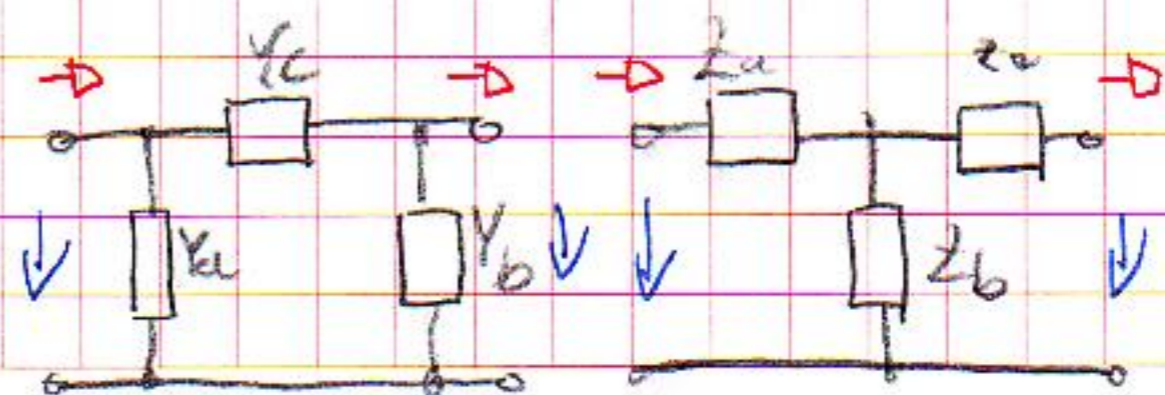

ideális távvezeték $\alpha = 0$ $\gamma = j\beta$

$$\left. \begin{aligned} U_1 &= U_2 \cos \beta l + I_2 Z_0 j \sin \beta l \\ I_1 &= \frac{U_2}{Z_0} \sin \beta l + I_2 \cos \beta l \end{aligned} \right\} Z_{in} = Z_0 \frac{Z_2 + j Z_0 \tan \beta l}{Z_0 + j Z_2 \tan \beta l}$$

távvezeték illesztés:

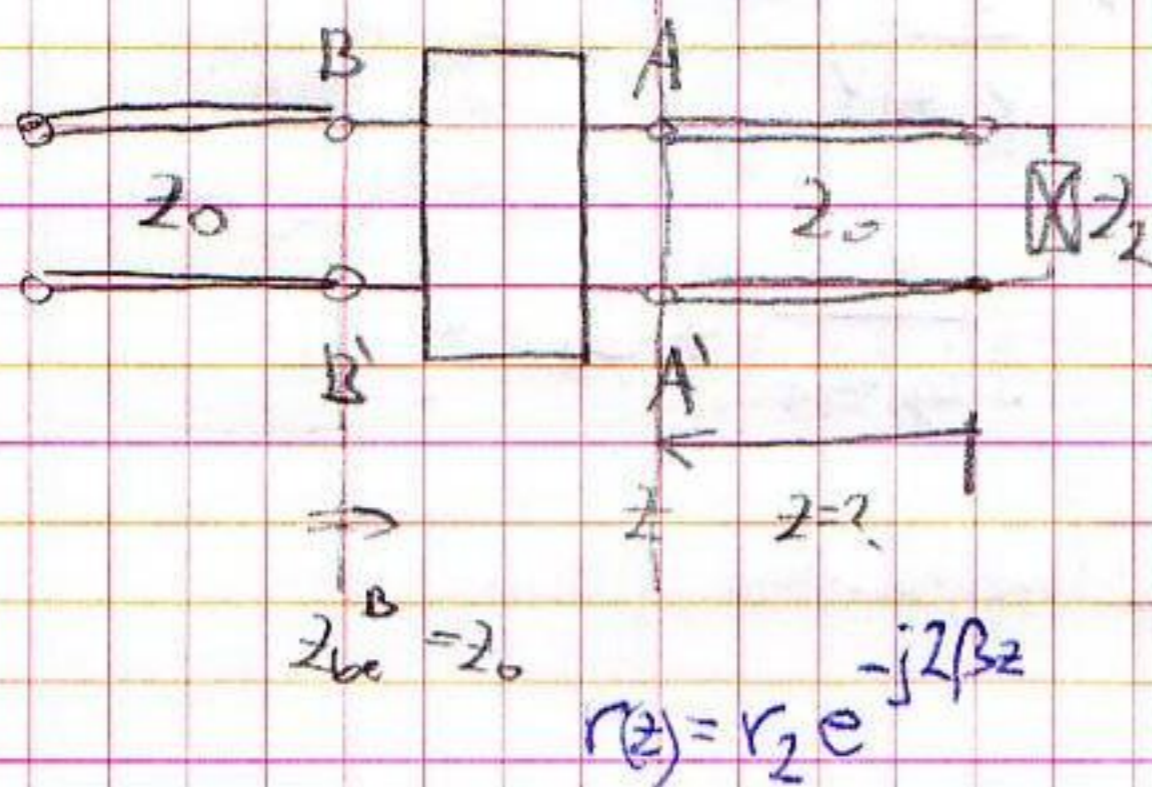

$$r(z) = 0 \quad VSWR = \frac{1 + |r(z)|}{1 - |r(z)|} = 1$$

$$U(z) = U_2^+ (e^{jz} + r(z) e^{-jz})$$


$$I(z) = \frac{U_2^+}{Z_0} (e^{jz} - r(z) e^{-jz})$$

$$Z_{in}^B(z) = Z_0$$

$$\Rightarrow z = l$$

$$Z_{in}^A(z) = Z_0 \frac{Z_2 + j Z_0 \tan \beta z}{Z_0 + j Z_2 \tan \beta z}$$

a) illesztés soros vonalal

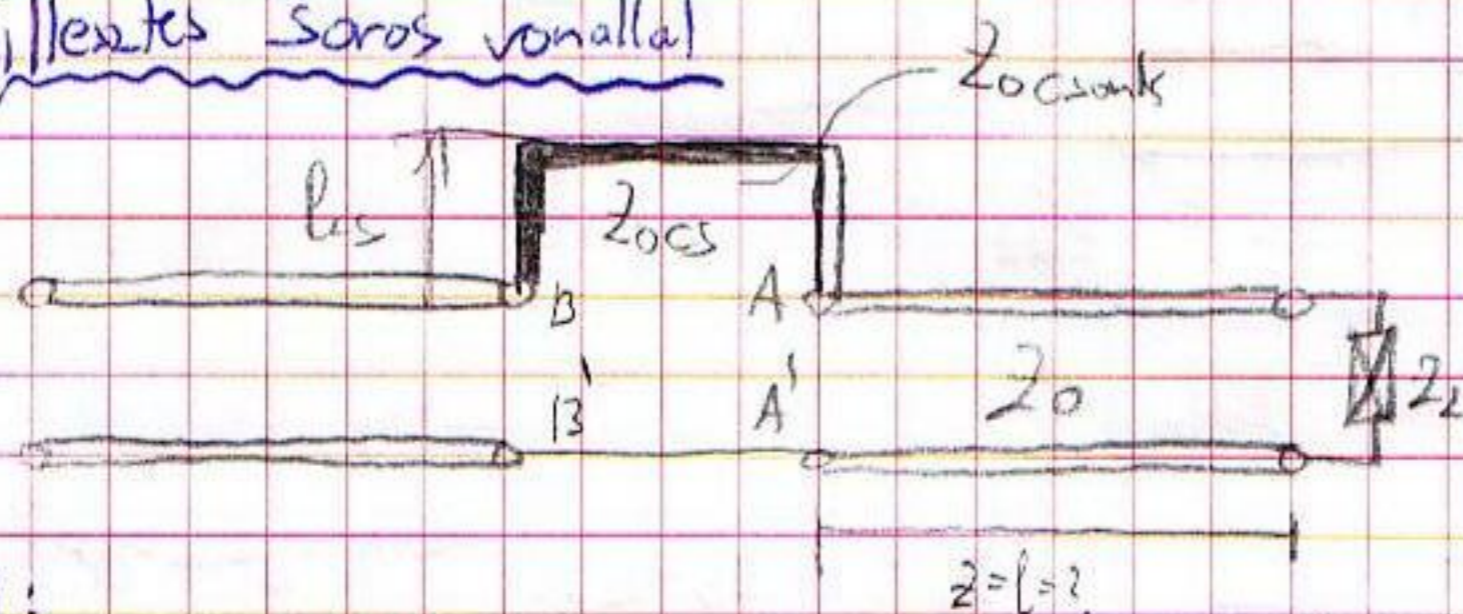

$$Z_{cs}^{be} = Z_{ocs} j \tan \beta l_{cs} = j X_{cs}$$

$$Z_{AA'}^{be} = Z_0 \frac{Z_2 + j Z_0 \tan \beta l}{Z_0 + j Z_2 \tan \beta l} =$$

$$= R_{AA'} + j X_{AA'}$$

$$Z_{BB'}^{be} = Z_0 = Z_{cs}^{be} + Z_{AA'}^{be} =$$

$$= j X_{cs} + R_{AA'} + j X_{AA'} = Z_0$$



feltétel:

$$\text{Im: } X_{cs} + X_{AA'} = 0$$

$$\text{Re: } R_{AA'} = 0 \Rightarrow z = l \text{ megválasztás}$$

ideális távvezeték, mint rezgőkör

a) rövidzár

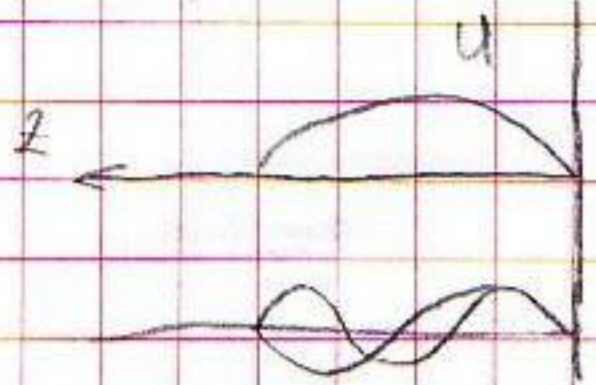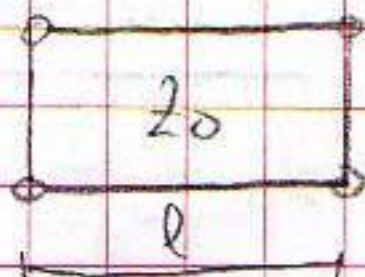



$$\frac{u_g}{2} \quad n=1$$

$$u_g = \frac{2l}{n} \quad n=1,2,\dots$$

$$f = \frac{v}{u_g} = \frac{c}{\sqrt{\mu_r \epsilon_r}} \cdot \frac{n}{2l}$$

Távvezeték saját frekvenciája


b) üresjárás (szekelős)

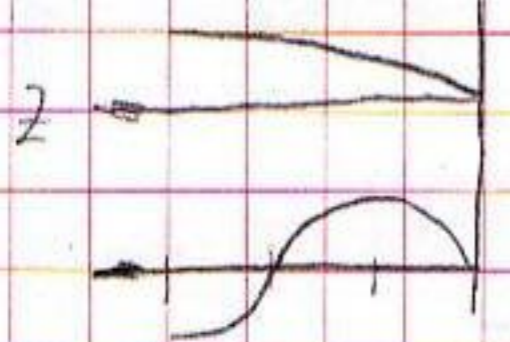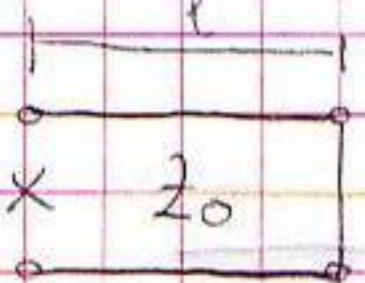

$$\frac{u_g}{4} (2n+1) = l$$

$$u_g = \frac{4l}{2n+1} \quad n=0,1,2,\dots$$

c/1) soros rezonancia

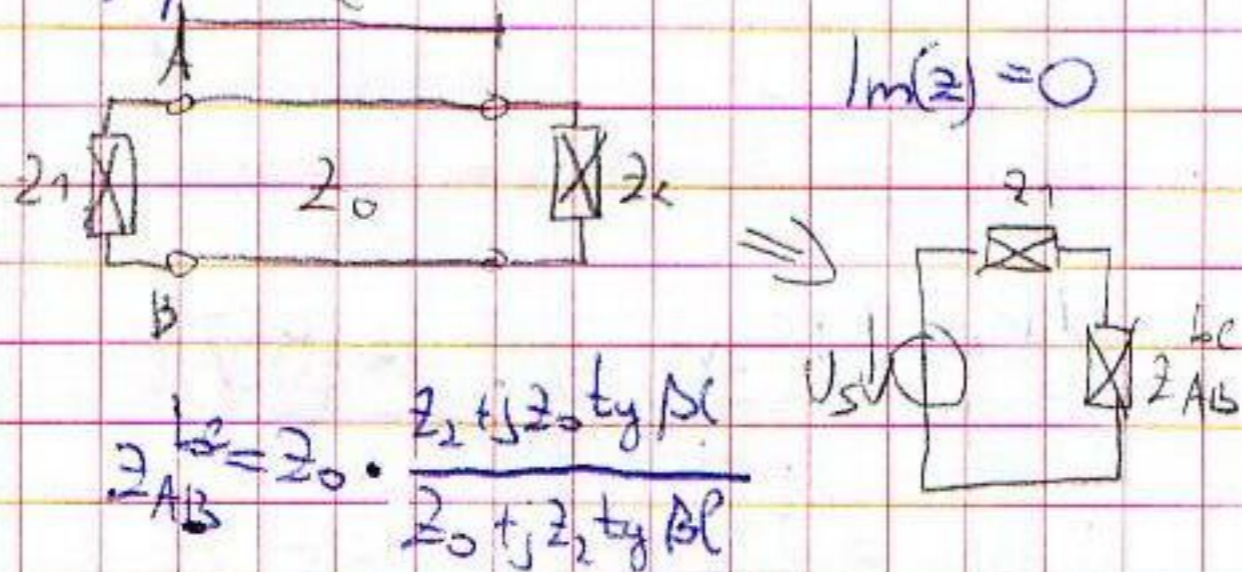

$$z_{AB}^{bc} = z_0 \cdot \frac{z_1 + jz_0 \tan \beta l}{z_0 + jz_1 \tan \beta l}$$

$$\text{Im}\{z_1 + z_{AB}^{bc}\} = 0 \Rightarrow l = \dots \quad (f \text{ adott})$$


$$f = \dots \quad (l \text{ adott})$$

c/2) párhuzamos rezonancia

$$\text{Im}(Y) = 0$$

$$\text{Im}\{Y_1 + Y_{AB}^{bc}\} = 0$$

példa (1)

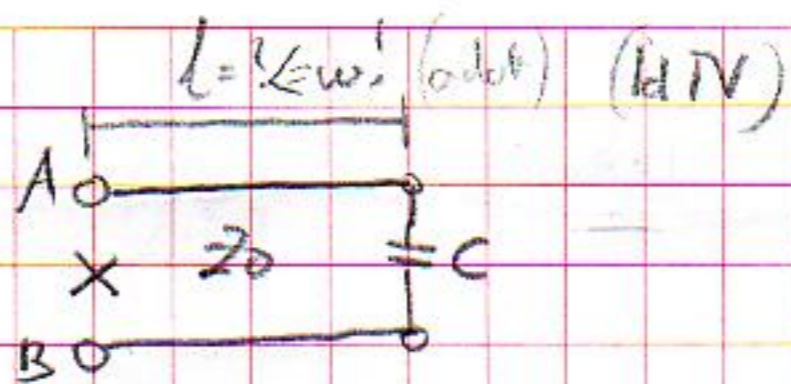


$$\text{Im } Z_{er} = \infty = Z_1(\infty) + Z_{AB} = Z_0 \frac{Z_2 + jZ_0 \tan \beta l}{Z_0 + jZ_2 \tan \beta l} = Z_0 \frac{\frac{1}{j\omega C} + jZ_0 \tan \beta l}{Z_0 + j \frac{1}{j\omega C} \tan \beta l}$$

$$\Rightarrow \text{elég a nevező} = 0 \quad Z_0 + \frac{1}{\omega C} \tan \beta l = 0$$


$$\Rightarrow \tan \beta l = -Z_0 \omega C$$

$$\beta l = \arctan(-Z_0 \omega C)$$
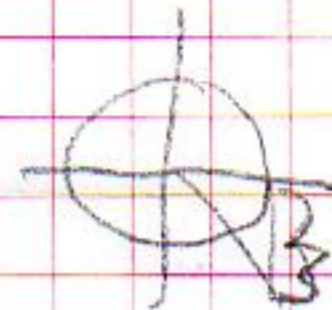
$$\frac{2\pi}{\lambda} \cdot l = \dots \Rightarrow l = \dots$$




példa (2)

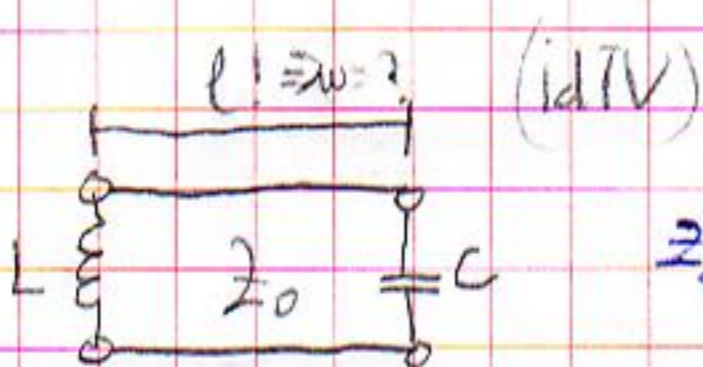

$$Z_{soros} = j\omega L + Z_0 \frac{\frac{1}{j\omega C} + jZ_0 \tan \beta l}{Z_0 + j \frac{1}{j\omega C} \tan \beta l}$$

$$\text{Im}(Z_{soros}) = 0 = \left(\omega L + \frac{Z_0}{\omega C} + \frac{Z_0^2 \tan \beta l}{Z_0 + \frac{1}{\omega C} \tan \beta l} \right) \Rightarrow \beta l = ?$$

Távvezeték transzienselv:

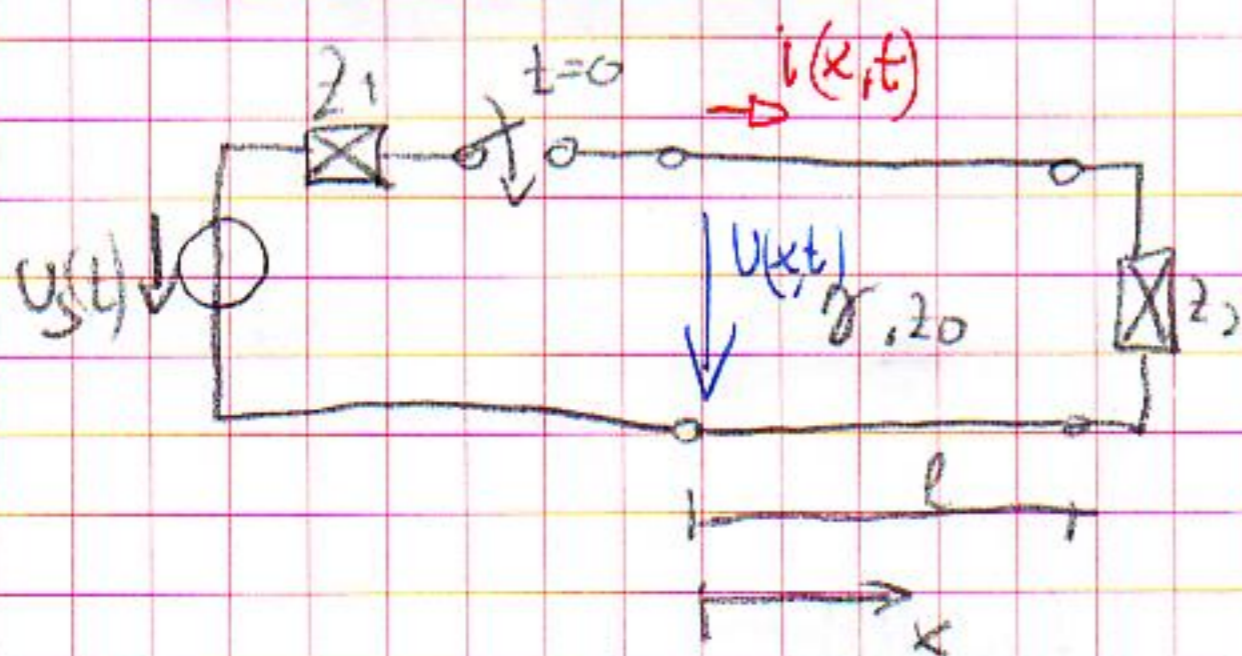

húldó + visszert

$$u(x,t) = f_1\left(t - \frac{x}{v}\right) + f_2\left(t + \frac{x}{v}\right)$$

$$i(x,t) = \frac{f_1\left(t - \frac{x}{v}\right)}{Z_0} - \frac{f_2\left(t + \frac{x}{v}\right)}{Z_0}$$

a) kezdeti érték feladat

$$t=0 \quad \left. \begin{aligned} u(x,0) = U(x) = f_1(x) + f_2(x) \\ i(x,0) = I(x) = \frac{f_1(x)}{Z_0} - \frac{f_2(x)}{Z_0} \end{aligned} \right\} \begin{aligned} f_1(x) &= \frac{1}{2} [U(x) + Z_0 I(x)] \\ f_2(x) &= \frac{1}{2} [U(x) - Z_0 I(x)] \end{aligned}$$

$$u(x,t) = \frac{1}{2} \left[\underbrace{U\left(t - \frac{x}{v}\right) + z_0 I\left(t - \frac{x}{v}\right)}_{f_1} + \underbrace{U\left(t + \frac{x}{v}\right) - z_0 I\left(t + \frac{x}{v}\right)}_{f_2} \right]$$


$$i(x,t) = \frac{1}{2z_0} \left[U\left(t - \frac{x}{v}\right) + z_0 I\left(t - \frac{x}{v}\right) - U\left(t + \frac{x}{v}\right) + z_0 I\left(t + \frac{x}{v}\right) \right]$$

b) peremített feladat

$$x=0 \quad U_s \quad \left. \begin{aligned} u(0,t) = U_0(t) = f_1(t) + f_2(t) \\ i(0,t) = I_0(t) = \frac{f_1(t)}{z_0} - \frac{f_2(t)}{z_0} \end{aligned} \right\} \begin{aligned} f_1(t) &= \left[U_0(t) + z_0 I_0(t) \right] \cdot \frac{1}{2} \\ f_2(t) &= \frac{1}{2} \left[U_0(t) - z_0 I_0(t) \right] \end{aligned}$$

$$u(x,t) = \frac{1}{2} \left[U_0\left(t - \frac{x}{v}\right) + z_0 I_0\left(t - \frac{x}{v}\right) + U_0\left(t + \frac{x}{v}\right) - z_0 I_0\left(t + \frac{x}{v}\right) \right]$$

c) Menetdiagramm

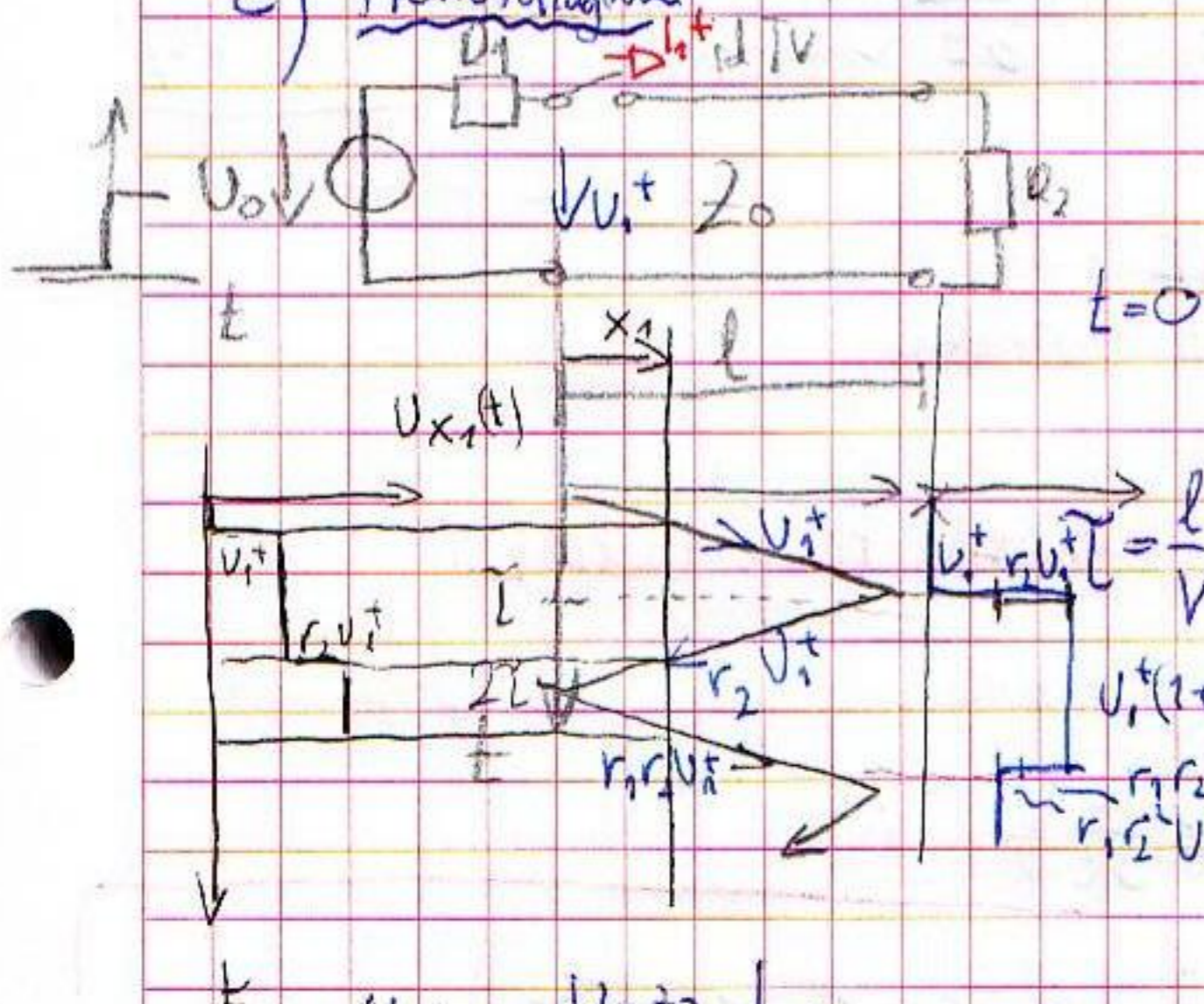

$$U_0 = R_1 I_1^+ + U_1^+ = U_1^+ \left(\frac{R_1}{z_0} + 1 \right)$$

$$\frac{U_1^+}{I_1^+} = z_0$$

$$U_1^+ = U_0 \frac{z_0}{R_1 + z_0}$$

$$r_2 = \frac{R_2 - z_0}{R_2 + z_0}$$

$$r_1 = \frac{R_1 - z_0}{R_1 + z_0}$$

$$U_2(\infty) = \frac{U_0 z_0}{z_0 + R_1} \left(1 + r_2 + \frac{r_1 r_2}{1+r_2} + \frac{r_1 r_2^2}{1+r_2} + \frac{r_1^2 r_2}{1+r_2} + \dots \right) = U_0 \left(\frac{z_0}{z_0 + R_1} \right) (1+r_2) \left(1 + r_1 r_2 + (r_1 r_2)^2 + \dots \right)$$

$$= U_0 \frac{z_0}{z_0 + R_1} \frac{(1+r_2)}{1-r_1 r_2} = \dots = U_0 \frac{R_2}{R_1 + R_2}$$