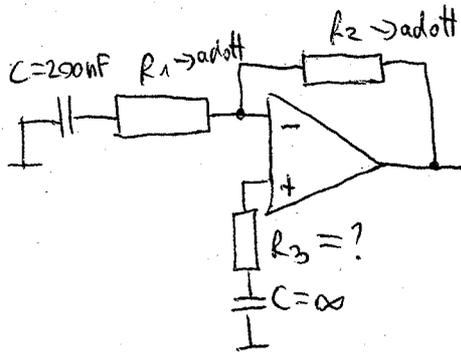



1.



$R_3 = ?$
 $A_{u_{DC}} = ?$
 $A_{u_{1kHz}} = ?$
 $f_0 = ?$

Milyen visszacsatolás ez?


2.

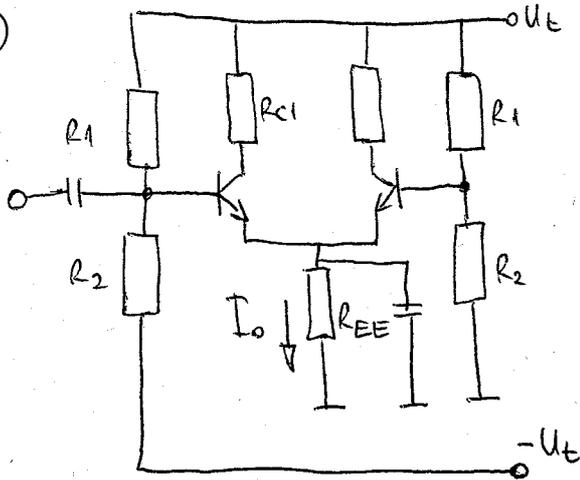

Ellenállásol adottal; β adott, $\pm U_E$ ismertel.

$I_0 = ?$
 ~~$R_{be} = ?$~~
 $A_u = ?$
 $R_{be} = ?$
 $R_{ki} = ?$

3.

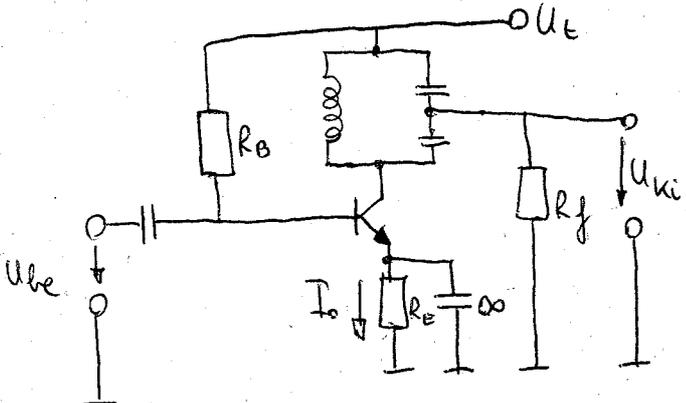

Adott: β , α ω R , C_1 , C_2 , f_0

$I_0 = ?$
 $L = ?$
 ~~$R_{be} = ?$~~
 $\beta_E = ?$
 $Q_E = ?$
 $A_u = ?$
 $R_{be} = ?$